

CLAMPER

A clamper is an electronic circuit that changes the DC level of a signal to the desired level without changing the shape of the input signal.

Types of clamper \Rightarrow

- It's of 3 types :-
- a) Positive
 - b) Negative
 - c) Biased

* The clamper is otherwise known as level shifter or DC restorer.

* Steps to solve clamper circuit \Rightarrow

\hookrightarrow Start the analysis by considering the input half-cycle which makes the diode forward biased.


\hookrightarrow During that half, capacitor will store its maximum charge. Then calculate capacitor voltage (V_C) and output voltage (V_O).

\hookrightarrow During another half, diode is reverse biased (open). Hence, capacitor will try to discharge the previously stored charge to the other component.

\hookrightarrow The ~~input~~^{output} voltage should be equal to input voltage.

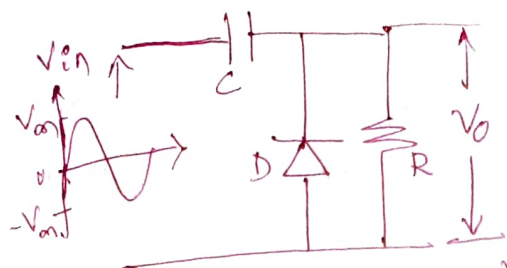a) Positive Clamper \Rightarrow It shifts the input signal towards the positive side or upward.

\hookrightarrow circuit consists of a diode, a resistor and a capacitor.




(Positive clamper)

During -ve half cycle, diode is forward biased. So, the capacitor will store its max.

By applying the loop eqⁿ in i/p side,

$$-V_{in} + V_C + V_D = 0$$
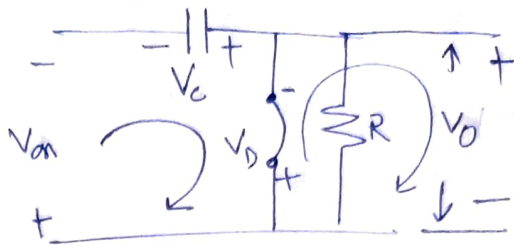
$$\Rightarrow V_C = V_{in} \quad (\text{if } V_D = 0) \quad (\text{Ideal diode is used})$$




(a)

By applying loop eqⁿ in o/p side,

$$-V_D - V_o = 0 \Rightarrow V_o = V_D = 0 \Rightarrow \text{for -ve half.}$$

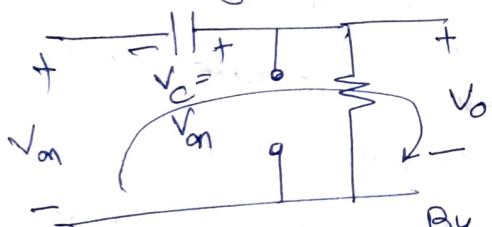During +ve half-cycle, diode is reverse biased. Hence signal appears at the output as shown in fig (b).



(b)

Input current directly flows towards the output.

By applying loop eqⁿ,

$$V_{in} + V_C - V_o = 0$$


$$\Rightarrow V_{in} + V_{in} = V_o$$

$$\Rightarrow V_o = 2V_{in} \rightarrow \text{for +ve half}$$

for sine & Δ wave,
Baseline = +ve half V_o +
negative half V_o

for this


$$= \frac{2V_{in}}{2} = V_{in}$$

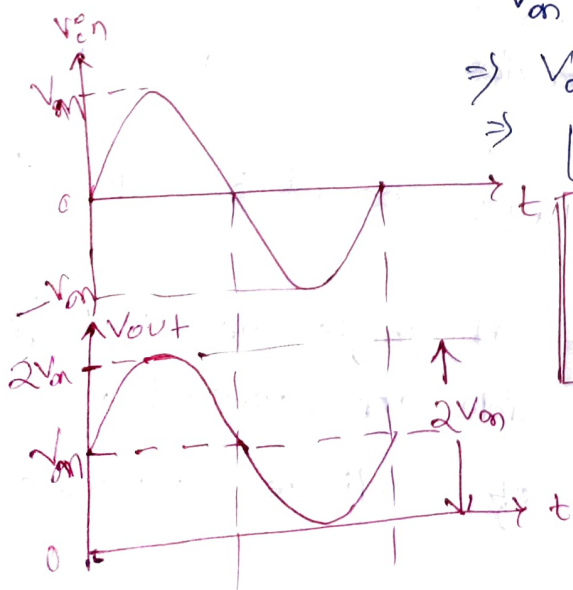

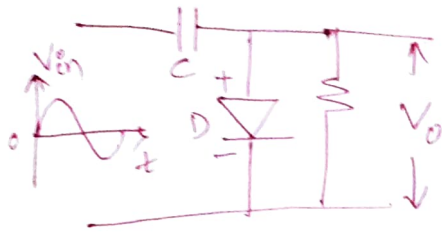b) Negative clamper


It shifts the waveform to negative side.

During +ve half cycle, diode is forward biased.




$$V_{in} - V_C - V_D = 0$$

$$\Rightarrow V_{in} = V_C$$

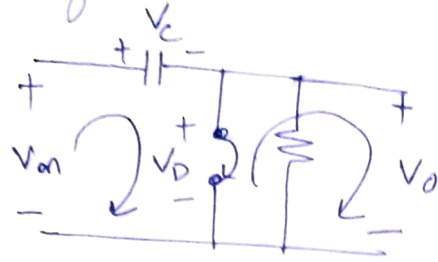

$$V_D - V_o = 0 \Rightarrow V_o = V_D = 0$$

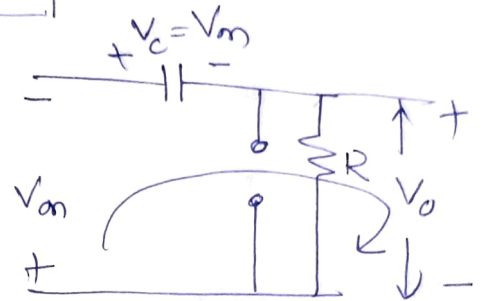During -ve half cycle, Diode is reverse biased and hence the signal appears at the output.




→ Diode does not allow current through it. The charge stored in capacitor is discharged.

$$-V_{in} - V_C - V_o = 0 \Rightarrow V_o = -V_{in} - V_C$$

$$= -V_{in} - V_{in}$$

$$V_o = -2V_{in}$$

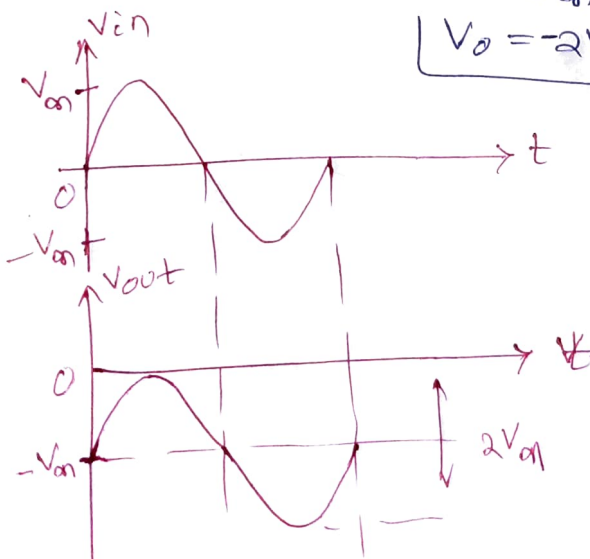

Base line =

$$\frac{0 - 2V_{in}}{2} = -V_{in}$$

Applications:-

- ↳ Used as dc restorer
- ↳ as voltage multipliers
- ↳ for protection of amplifier

↳ used as base-line Stabilizer