



# G. I. E. T. UNIVERSITY

GUNUPUR, Dist-Rayagada(O)

## CONTENTS

Sl.No.	Date	Name of the Experiment	Page No.	Remarks
01	07/02/25	To Study about different electronic components and devices.	1 - 7	Raw 21/2/25
02	21/02/25	To Study about ohm's law and realize the relationship between voltage and current	08-10	Raw 25/2/25
03	28/02/25	Study and use of oscilloscope and signal generators to view waveforms and measure amplitude and frequency of a given wave form	11-15	Raw 4/3/25
04	04/03/25	To verify Thevenin's theorem in a DC network.	16-19	Raw 12/03/25
05	25/02/25	To Study the V-I Characteristics graph of P-N junction diode.	20-22	Sandus 4/3/25
06	04/03/25	To study about the Half-wave & Full-wave rectifier circuits with and without capacitor filters and recording the output waveforms	23-25	Raw 14/03/25
07	11/03/25	Measurement of current voltage power factor in series R-L-C circuit excited by a single phase AC supply	26-28	Raw 18/03/25
08	18/03/25	power factor measurement for fluorescent lamp	29-31	Raw 25/03/25
09	08/04/25	To study and verify different logic gates.	32-33	



SEMESTER

# G. I. E. T. UNIVERSITY

GUNUPUR

2<sup>nd</sup>

SHEET NO.

01

## EXPERIMENT NO. :-1

### AIM OF THE EXPERIMENT:-

TO STUDY about different electronic components and devices.

### OBJECTIVE:-

Familiarization of electronic components such as Resistor, capacitor, Bread board, LEDs, ICS, Diode, Transistors etc. Testing and measurement of component values using digital multimeter.

### COMPONENTS REQUIRED:-

Digital multi meter  
Different Component :- Resistor, Diode, capacitor and transistor.

### THEORY:-

#### RESISTOR:-

Most axial resistors use a pattern of colored strips to indicate resistance. A "4 band" identification is the most commonly used color coding scheme on all resistors. It consists of four color bands that are painted around the body of the resistor.



NAME Rajesh Rana

UNIV. ROLL \_\_\_\_\_

1101101

# EXPERIMENT NO. -

- 10.001 THE RESISTOR

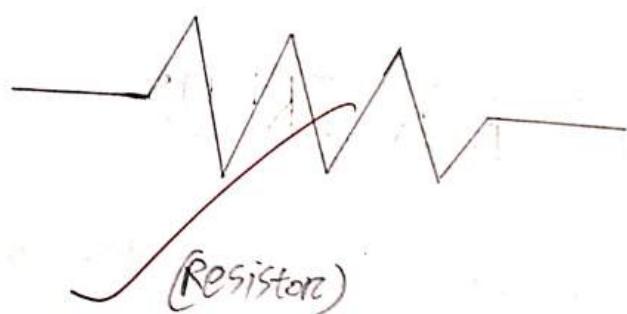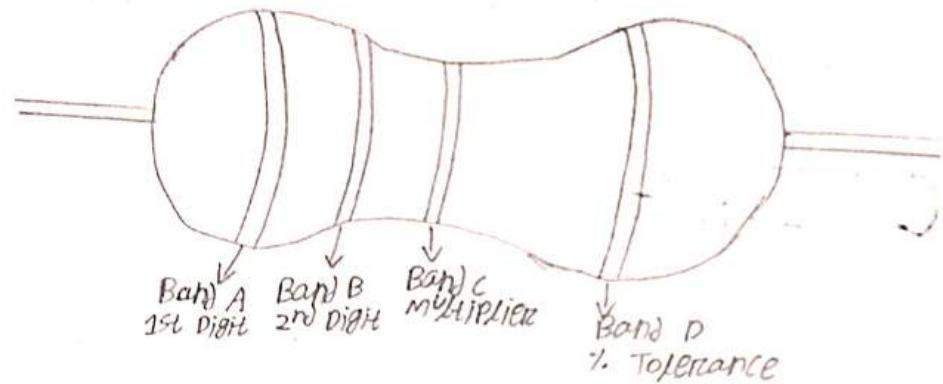

✓ (Resistor)

- 11. THE DIODE



SEMESTER

2<sup>nd</sup>

# G. I. E. T. UNIVERSITY

## GUNUPUR

SHEET No.

02

Resistor values are always coded in "Ohms" ( $\Omega$ ).



Color	Digit	Multiplier	Tolerance (%)
Black	0	$10^0$ (1)	
Brown	1	$10^1$	1
Red	2	$10^2$	2
orange	3	$10^3$	
Yellow	4	$10^4$	
Green	5	$10^5$	0.5
Blue	6	$10^6$	0.25
Violet	7	$10^7$	0.1
Grey	8	$10^8$	
white	9	$10^9$	
Gold		$10^{-1}$	5
Silver		$10^{-2}$	10
(none)			20

## CAPACITOR:-


A capacitor is a device which stores electrical charge. A basic capacitor has two parallel plates separated by an insulating material.

The unit of capacitor is "Farad" (F).

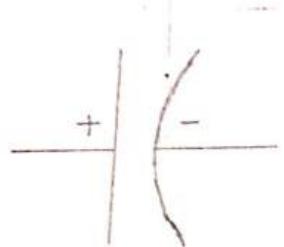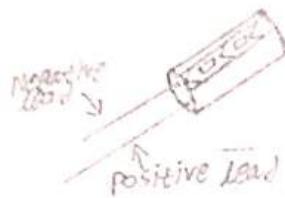Capacitance values are normally smaller such as  $\mu\text{F}$ ,  $\text{nF}$ ,  $\text{pF}$ .



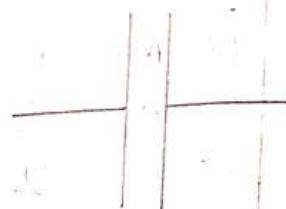
Polarized Electrolytic capacitor  
and its electric symbol



Non-polarized ceramic capacitor  
and its electric symbol

(Diode)

- IGT I 1990

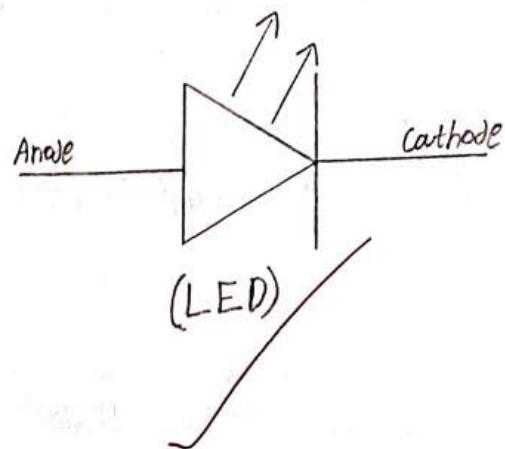



# G. I. E. T. UNIVERSITY

GUNUPUR

SEMESTER

2<sup>nd</sup>

SHEET No.

03

Electrolytic Capacitor:- An electrolytic capacitor is a type of capacitor that uses an electrolyte, an ionic conducting liquid, as one of its plates, to achieve a larger capacitance per unit volume than other types. They are used in relatively high current and low frequency electrical circuits.

Ceramic Capacitor:- These capacitors are generally non polarized and almost as common as radial electrolyte capacitors. Generally, they use an alpha numeric marking system. The number of part is the same as resistor except that the value represented is in pF. They may also be written out directly for instance  $2n2 = 2.2\text{ nF}$ .

## BREAD BOARD:-

A bread board is used to build and test circuits quickly before finalizing any circuit design. The bread board has many holes into which circuit components like ICs and Resistors can be inserted. A typical bread board.

## LED:-


A light emitting diode (LED) is a semiconductor device that emits light when an electric current is passes through it. Light is produced when the particles that carry the current (known as electrons and

UNIV. ROLL \_\_\_\_\_



NAME Rajesh Rana

COLL. ROLL 24CSEAIML025

DATE 07/01/25

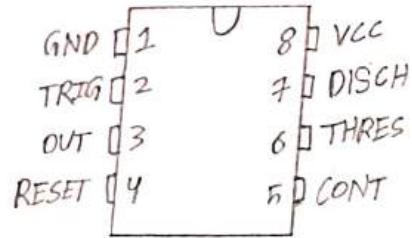

INTEGRATED CIRCUIT (IC)

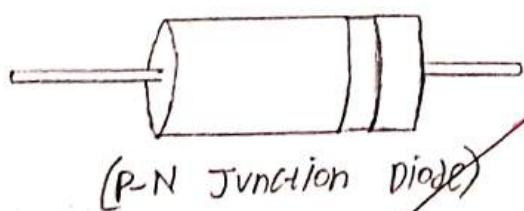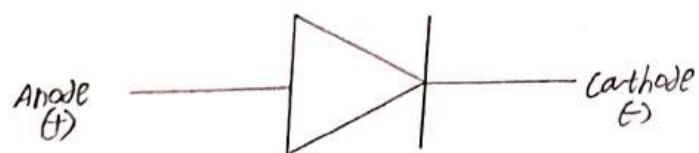



SEMESTER

# G. I. E. T. UNIVERSITY

## GUNUPUR

2<sup>nd</sup>

SHEET NO.

04

(holes) combines together with in the semi conduction material.

## INTEGRATED CIRCUIT (IC):-

An integrated circuit (IC) is a small semiconductor based electronic device consisting of fabricated transistors, resistors and capacitors. Integrated circuits are the building blocks of most electronic devices and equipment.

An integrated circuit also known as chip or microchip.



## DIODE:-

A diode is a specialized electronic component with two electrodes called the anode and the cathode.

Diodes are basic unidirectional semiconductor devices that will only allow current to flow through them in one direction only.



Semiconductor Diode: - A p-n junction diode is a two terminal devices, which allows the electric current in only one direction which block the electric current in opposite or reverse direction. If the diode is forward biased, it allows the electric current flow on the other hand if the diode is reverse biased it blocks the electric current flows. P-N junction semiconductor device.

UNIV. ROLL \_\_\_\_\_

NAME Rajesh Rana

COLL. ROLL 2YCSEAIML015

DATE 07/01/25

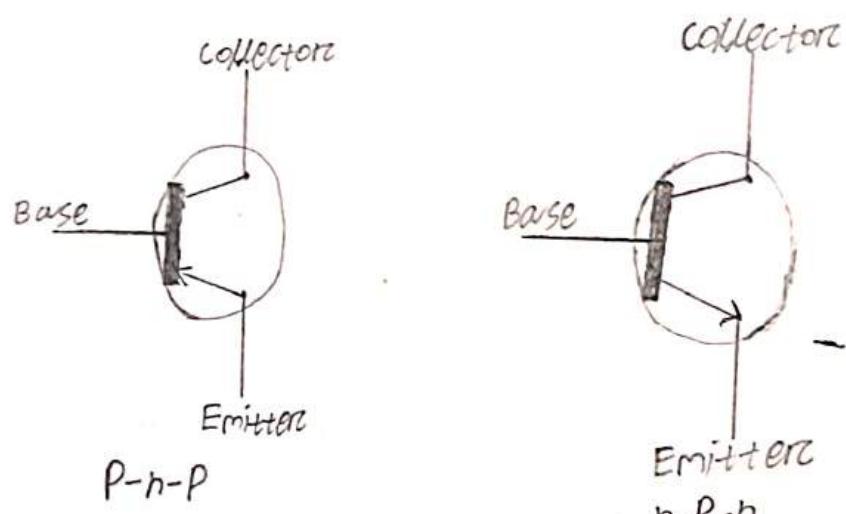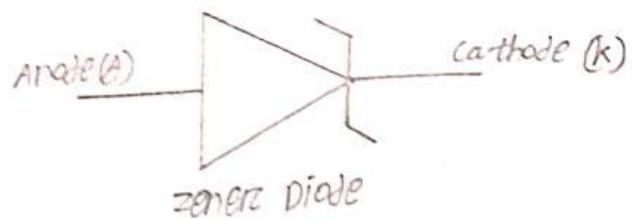

(TRANSISTOR)



# G. I. E. T. UNIVERSITY

## GUNUPUR

SEMESTER

2<sup>ND</sup>

SHEET No. 05

Zener Diode:- A heavily doped semiconductor diode which is designed to operate in reverse direction is known as the zener diode. In other words, the diode in which specially designed for optimizing the break down region is known as the zener diode.

## TRANSISTOR:-

A transistor is a semiconductor device used to amplify or switch electronic signals and electrical power. It is composed of semi conduction material usually with at least three terminals for connection to an external circuit.

The transistor has three terminals named as Emitter, Collector and Base.

The Transistor is of two types:-

- (a) N-P-N type
- (b) P-N-P type


(a) N-P-N type:- The transistor in which one P-type material is placed between two N-type material is known as N-P-N transistor. In N-P-N transistor the direction of movement of an electron is from the emitter to collector (current is from collector to emitter) region due to which the current constitutes in the transistor.

UNIV. ROLL \_\_\_\_\_


NAME \_\_\_\_\_ Rajesh Rana

COLL. ROLL 2YCSEAIML025

DATE 07/01/25

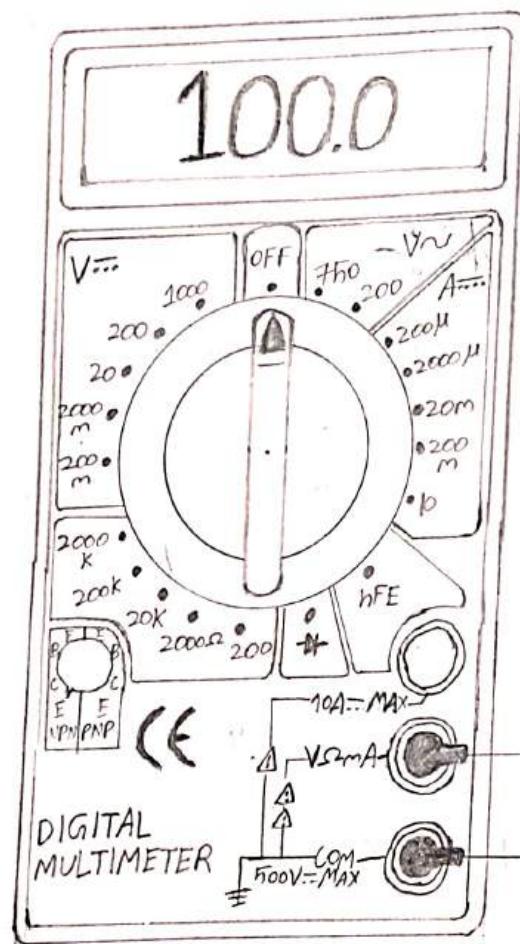

(MULTIMETER)

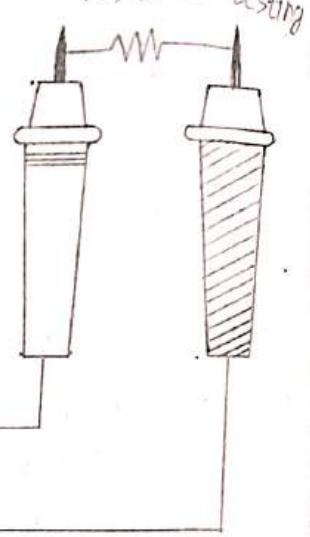

W-9-W



SEMESTER

2<sup>nd</sup>

# G. I. E. T. UNIVERSITY

## GUNUPUR

SHEET No. 06

(b) P-N-P type:- The transistor in which one N-type material is placed between two P-type materials is known as P-N-P transistor. In P-N-P transistor the direction of movement of an electron is from the collector to emitter (current is from emitter to collector) region due to which the current constitutes in the transistor.

### MULTIMETER:-

A digital multi meter (DMM) is a test tool used to measure two or more electrical values principally voltage (Volts), current (amps) and resistance (ohms). It is a standard diagnostic tool for technicians in the electrical / electronic industries.

### TABULATION :-

#### RESISTOR:-

SL. No.	Colour of rings				True value ( $\Omega$ )	Measured value ( $\Omega$ )	% of Error
	1	2	3	4			
1	Brown	Black	orange	Silver	$10k\Omega \pm 10$	$10.34k\Omega$	3.4
2	Red	Red	Yellow	Golden	$220k\Omega \pm 5$	$23.2k\Omega$	5.45
3	Yellow	violet	Brown	Golden	$470\Omega \pm 5$	$460\Omega$	-2.12
4	Brown	Black	Black	Golden	$10\Omega \pm 5$	$16\Omega$	9.1

UNIV. ROLL \_\_\_\_\_

COLL. ROLL 24/CSEATM1 \_\_\_\_\_

NAME \_\_\_\_\_



SEMESTER

2<sup>nd</sup>

# G. I. E. T. UNIVERSITY

GUNUPUR

SHEET No. 07

## CAPACITOR:-

SL. NO.	TYPE OF CAPACITOR	TRUE VALUE ( $\mu F$ )	MEASURED VALUE ( $\mu F$ )
1	ELECTROLYTIC	100	123.1
2	ceramic	$10 \times 10^{-4}$	0.10

## DIODE:-

SL.NO.	TYPE OF DIODE	TRUE VALUE	MEASURED VALUE
1	LED		Glow
2	Zener Diode	0.7	814
3	Silicon Diode	0.7	600

## TRANSISTOR:-

SL. NO.	TYPE OF TRANSISTOR	GRAN (β)
1	PNP	306
2	NPN	462

## CONCLUSION:-

In this experiment we have studied about different component like resistor, capacitor, diode and transistor. and the percentage of error in resistor is 3.9575%.

~~Rajesh Rana  
07/01/25~~

UNIV. ROLL \_\_\_\_\_

NAME Rajesh Rana

COLL. ROLL 24CSEAIML015

DATE 07/01/25



SEMESTER

# G. I. E. T. UNIVERSITY

## GUNUPUR

2<sup>nd</sup>

SHEET No.

08

### EXPERIMENT NO. :- 2

Aim of the experiment:-

To study about Ohm's law and realize the relationship between voltage and current.

Apparatus Required:-

SL. NO	Name of the experiment	Range	TYPE	Quantity
1	Ammeterz	0-1A AC	MI	1
2	Voltmeterz	0-300V AC	MI	1
3	Incandescent lamp	230V, 200W	WW	1
4	Connecting wires	230V, 5A, $\frac{1}{8}$ PVC coated	AS PER REQUIREMENT	
5	Auto transformerz (Variac)	0-270V, 15A	WW	1


### Theory:-

There are two types of lamp which are in common use. One is filament lamp and the other is gaseous discharge lamp. The filament lamps are incandescent lamp. The filament of these lamps when heated due to electric current emits radiation of visible spectrum. The filament is mostly made up of tungsten wires whose melting point is  $3400^{\circ}\text{C}$  at normal.


UNIV. ROLL \_\_\_\_\_

NAME \_\_\_\_\_ Rajesh Rana

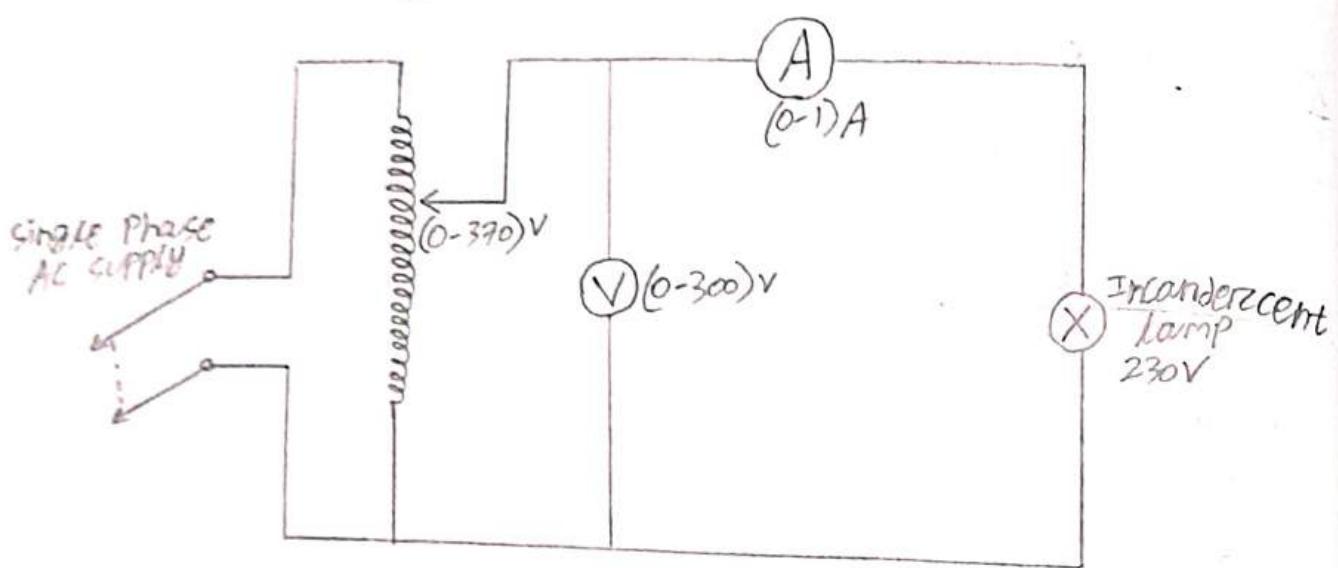COLL. ROLL 24CSEAIML015DATE \_\_\_\_\_ 21/01/25



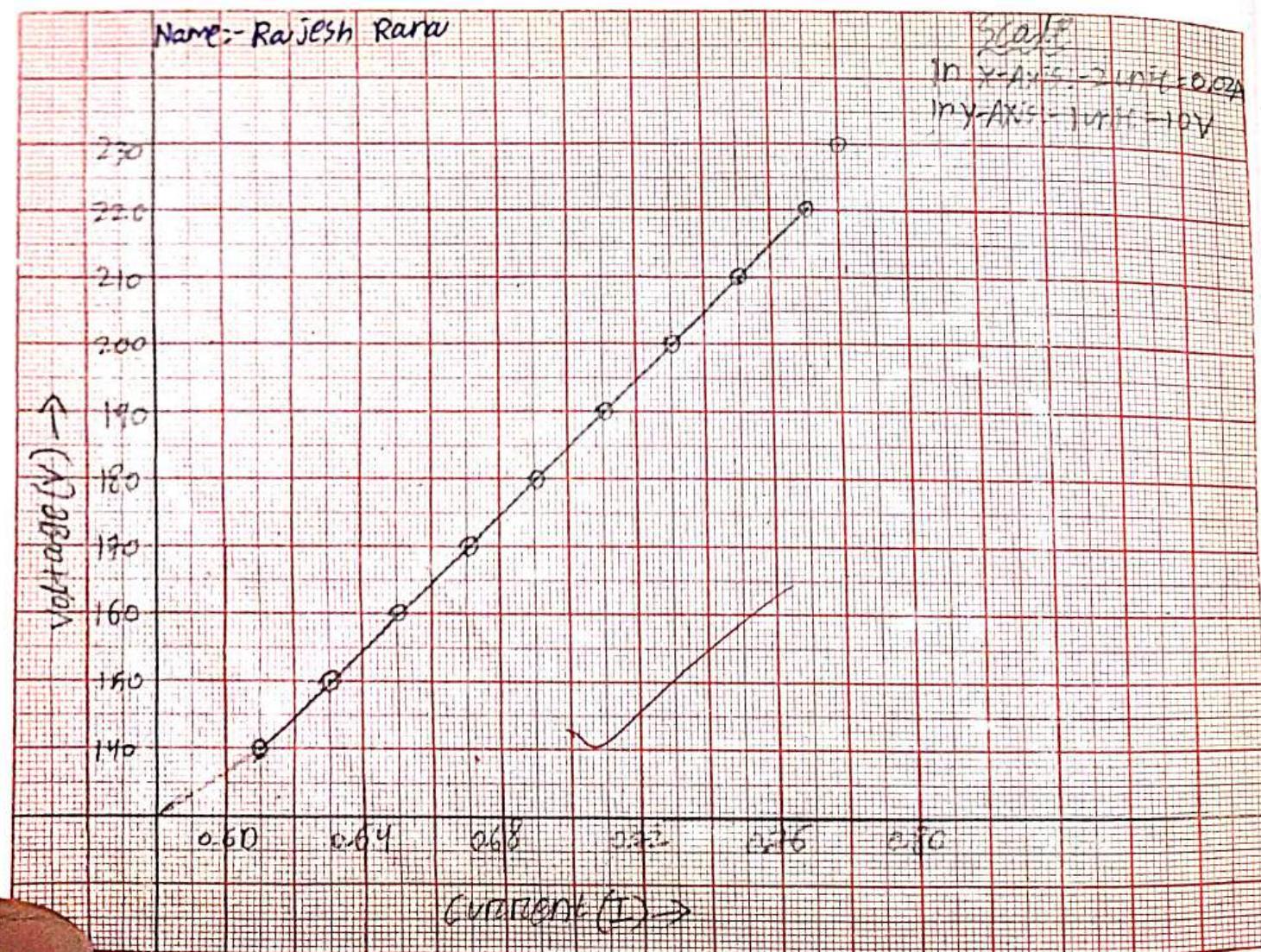(V-I) characteristic of  
Incandescent lamp





# G. I. E. T. UNIVERSITY

GUNUPUR

SEMESTER

2<sup>nd</sup>

SHEET No.

09

## Procedure :-

- i) The circuit is connected according to the circuit diagram.
- ii) By adjustment of Variac to 100V, the ammeter and voltmeter reading were taken.
- iii) The reading of voltage by vary in steps of 20 volt of voltmeter & ammeter were taken.
- iv) The voltage is varied up to 230 Volts and 10 reading were taken.
- v) The V-I graph has been drawn in the graph paper.

## Tabulation:-

SL.No	Voltmeter Reading	Ammeter Reading	$R = \frac{V}{I}$ in ohm
1	230	0.78	294.87
2	220	0.77	285.71
3	210	0.75	280.00
4	200	0.73	273.97
5	190	0.71	267.60
6	180	0.69	260.80
7	170	0.67	253.73
8	160	0.65	246.15
9	150	0.63	238.09
10	140	0.61	229.50

UNIV. ROLL \_\_\_\_\_

NAME Rajesh Rana

COLL. ROLL 24CSEAIML015

DATE 21/01/25



SEMESTER

# G. I. E. T. UNIVERSITY

## GUNUPUR

2<sup>nd</sup>

SHEET No.

10

mean Resistance,

$$R = \frac{\Sigma R}{10} = 263.048 \Omega$$

CONCLUSION:-

From the above observation table Vol I.

3PM  
28/11/25

UNIV. ROLL \_\_\_\_\_

NAME Rajesh RanaCOLL. ROLL 24CSEAIML015DATE 21/01/25



SEMESTER

2<sup>nd</sup>

# G. I. E. T. UNIVERSITY

## GUNUPUR

SHEET No.

21

Experiment No:- 3

### AIM OF THE EXPERIMENT:-

Study and use of oscilloscope and signal generator to view waveforms and measure amplitude and frequency of a given waveform.

### OBJECTIVE:-

- To introduce the basic structure of a cathode ray oscilloscope.
- To get familiar with the use of different control switches of the devices.
- To visualize an ac signal, measure the amplitude, frequency and time period.

### COMPONENTS REQUIRED:-

- Cathode Ray Oscillator (CRO)
- Function generator (FG)
- Connecting probes.

### THEORY:-

The cathode ray oscilloscope (CRO) is a common laboratory instrument that provides accurate time and amplitude measurements of voltage signals over a wide range of frequencies. Its reliability, stability and ease of operation make it suitable as a general purpose of laboratory instrument. A general purpose oscilloscope consists of the following parts:-

- cathode ray tube
- vertical amplifier
- delay line
- Time base generator

UNIV. ROLL \_\_\_\_\_

NAME Rajesh RanaCOLL. ROLL 24CSEAIML025DATE 27/01/25



# G. I. E. T. UNIVERSITY

GUNUPUR

SEMESTER

2<sup>nd</sup>

SHEET NO.

12

- Horizontal amplifier
- Trigger circuit
- Power supply

## CATHODE RAY TUBE:-

It is the heart of the oscilloscope when the electrons emitted by the electron gun strikes the phosphor screen, a visual signal is displayed on the CRT.

## VERTICAL AMPLIFIER:-

The input signals are amplified by the vertical amplifier. Usually the vertical amplifier is a wide band amplifier which passes the entire band of frequencies.

## DELAY LINE:-

As the name suggest, this circuit is used to delay the signal for a period of time in a vertical section of CRT. The input signal is not applied directly to the vertical plates because the part of the signal gets lost, when the delay time is not used. Therefore, the input signal is delayed by a period of time.

## TIME BASE GENERATOR:-



Time base circuit uses a uni-junction transistor, which is used to produce the sweep. The saw tooth voltage produced by the time base circuit is required to deflect the beam in the horizontal section. The saw tooth voltage at a constant time dependent rate.

UNIV. ROLL \_\_\_\_\_

NAME Rajesh Ranu

COLL. ROLL 24CSEAIMLOLH

DATE 27/07/25

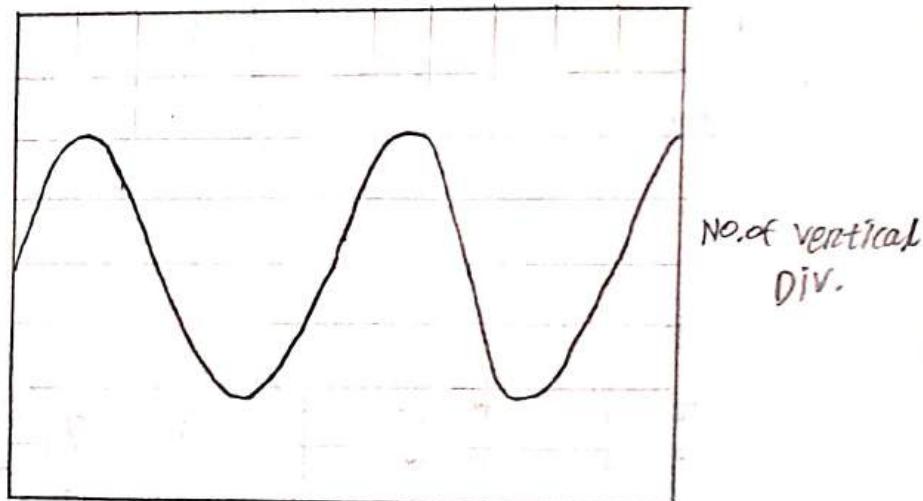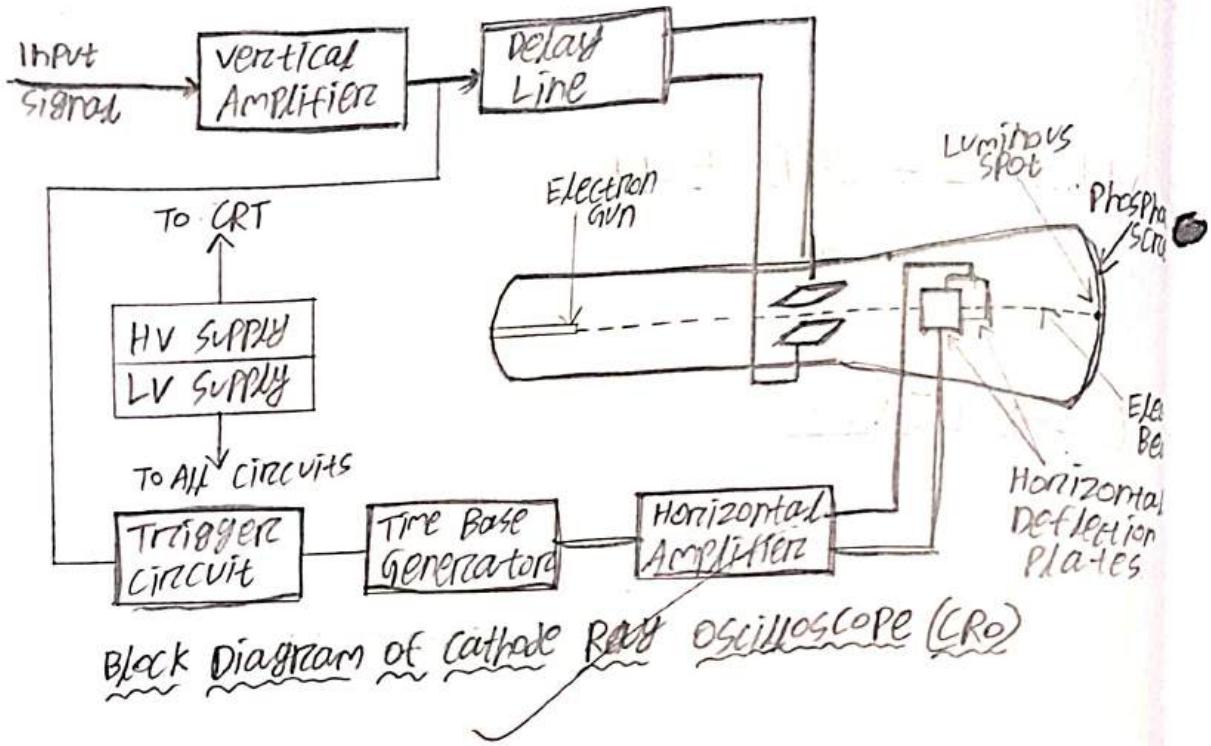



# G. I. E. T. UNIVERSITY

SEMESTER

2<sup>nd</sup>

GUNUPUR

SHEET NO.

23

## HORIZONTAL AMPLIFIER:-

The saw tooth voltage produced by the time base circuit is amplified by the horizontal amplifier before it is applied to horizontal deflection plates.

## TRIGGER CIRCUIT:-

The signals which are used to active the triggered circuit are converted to trigger pulses for the precision sweep operation whose amplitude is uniform. Hence, input signal and the sweep frequency can be synchronized.  
i.e. In a CRO, a triggering circuit is provided for synchronizing two types of deflection so that horizontal deflection starts at the same point of the input vertical signal each time it sweeps.

## PROCEDURE :-


- Turn on the oscilloscope.
- Adjust the intensity and focus of the trace.
- Use the X & Y knobs to centre the trace horizontally and vertically.
- Connect the cable from CH1 of the CRO to function generator.
- A signal will appear on the screen.
- Make sure that the inner red knobs of the volt/div and the time/div are locked clockwise.
- Set the frequency of the generator to 100Hz.
- Adjust the volt/div and time/div knobs so that you get a suitable size signal.
- Count the number of vertical squares fitting within the signal, then calculate the peak to peak values as:-  
 $VP-P = \text{No. of vertical div.} * \text{volt/divs.}$

UNIV. ROLL \_\_\_\_\_


NAME Rajesh Rana

COLL. ROLL 24CSEAIML075


DATE 27/07/25

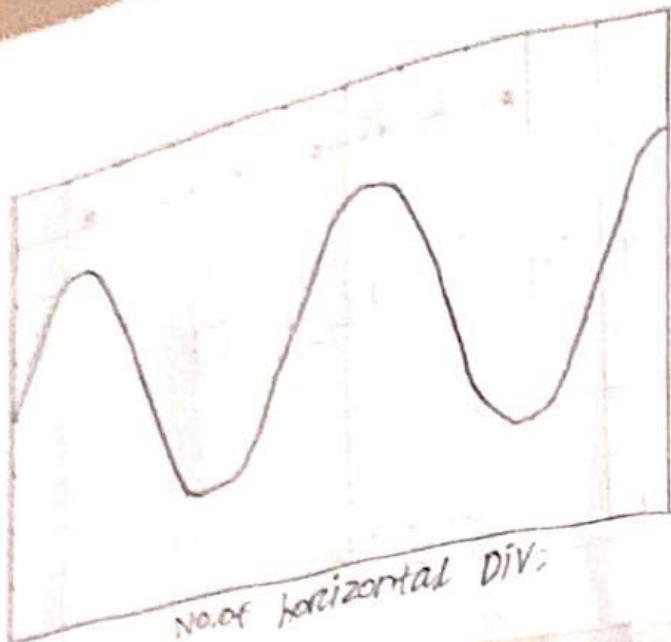

sine wave

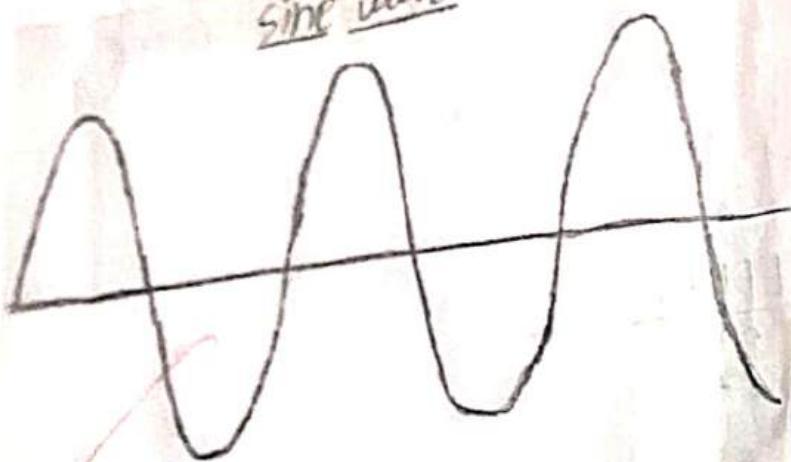

square wave

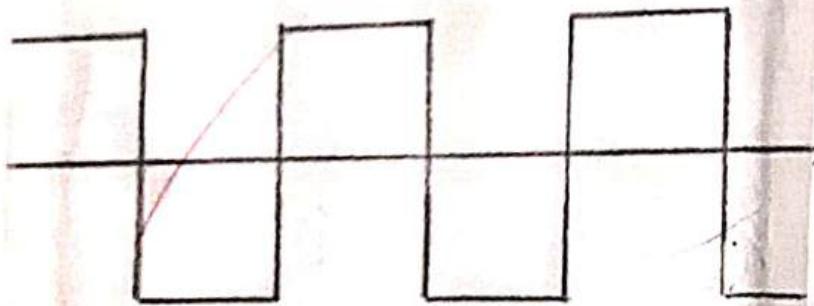

$a = 0.8V$   
 $T = 0.003698$   
 $f = 277.77 \text{ Hz}$



SEMESTER

# G. I. E. T. UNIVERSITY

## GUNUPUR

2<sup>nd</sup>

SHEET NO.

24

→ Count the number of horizontal squares fitting with in the duty cycle, then calculate time values as:-  
Time = No. of horizontal Div. \* Time / Divs.

→ Calculate the frequency of signal by using formula:-  
Frequency = 1/T. ✓

### CALCULATIONS:-

For Sine wave

$$\text{① Amplitude} = 13 \times 0.2 \times 0.2 = 0.52V$$

$$\text{② Time Period} = 18 \times 0.2 = 3.6 \times 10^{-3} = 0.0036 \text{ sec}$$

$$\text{③ Frequency} = 277.77 \text{ Hz} \quad \checkmark$$

For square wave

$$\text{① Amplitude} = 8 \times 0.5 \times 0.2 = 0.8V$$

$$\text{② Time Period} = 18 \times 0.2 = 3.6 \times 10^{-3} = 0.0036 \text{ sec}$$

$$\text{③ Frequency} = 277.77 \text{ Hz} \quad \checkmark$$


UNIV. ROLL \_\_\_\_\_

NAME \_\_\_\_\_ Ravish Rana

COLL. ROLL \_\_\_\_\_ 24CSEAIML025

DATE \_\_\_\_\_ 27/01/25

### Triangle wave

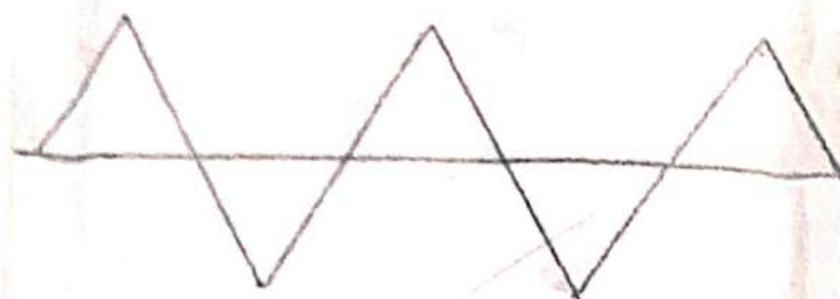

$$a = 0.8V$$

$$T = 0.046666\text{sec}$$

$$f = 219.391\text{Hz}$$



SEMESTER

# G. I. E. T. UNIVERSITY

**GUNUPUR**

2<sup>nd</sup>

SHEET No. 25

For Triangular wave:-

- (i) Amplitude =  $8 \times 0.5 \times 0.2 = 0.8 \text{ V}$
- (ii) Time Period =  $23 \times 0.2 = 4.6 \times 10^{-3} = 0.0046 \text{ SEC}$
- (iii) Frequency =  $277.39 \text{ Hz}$  ✓

OBSERVATIONS:-

SL NO.	TYPE OF WAVE	VOLTAGE (V)	TIME PERIOD (S)	Frequency(Hz)	
				Practical	Theory
1	Sine wave	0.52 V	0.0036 SEC	277.77 Hz	
2	Sawtooth wave	0.8 V	0.0036 SEC	277.77 Hz	
3	Triangular wave	0.8 V	0.0046 SEC	217.39 Hz	

CONCLUSION:-

We have measured amplitude, time period and frequency for the given wave form.

  
Rajesh Raha

UNIV. ROLL \_\_\_\_\_

NAME Rajesh RahaCOLL. ROLL 2YCSEAIML025DATE 27/02/25



# G. I. E. T. UNIVERSITY

**GUNUPUR**

2<sup>nd</sup>

SHEET NO.

26

## EXPERIMENT No:- 9

### AIM OF THE EXPERIMENT:-

To verify Thevenin's theorem in a DC network.

### APPARATUS REQUIRED:-

SL. No.	Components	TYPE	Rating	Quantity
1	Trainer Kit		0-15V	1
2	Ammeter	DC	250mA	1
3	Multi-Meter	Digital	0-99999	1
4	Patch chords	Double Ended	0.5W	As per Required



### THEORY:-

I am verifying Thevenin's theorem, which states that any linear network can be replaced by an equivalent voltage source ( $V_{th}$ ) in series with a resistance ( $R_{th}$ ). The voltage ( $V_{th}$ ) is the open-circuit voltage at the load terminals, and the resistance ( $R_{th}$ ) is the resistance of the network seen from the load terminals with all voltage sources replaced by their internal resistances.

To determine  $V_{th}$ , I follow these steps:

- I remove the load resistance.
- I measure the open-circuit voltage across the load terminals.

### CIRCUIT DIAGRAM:-

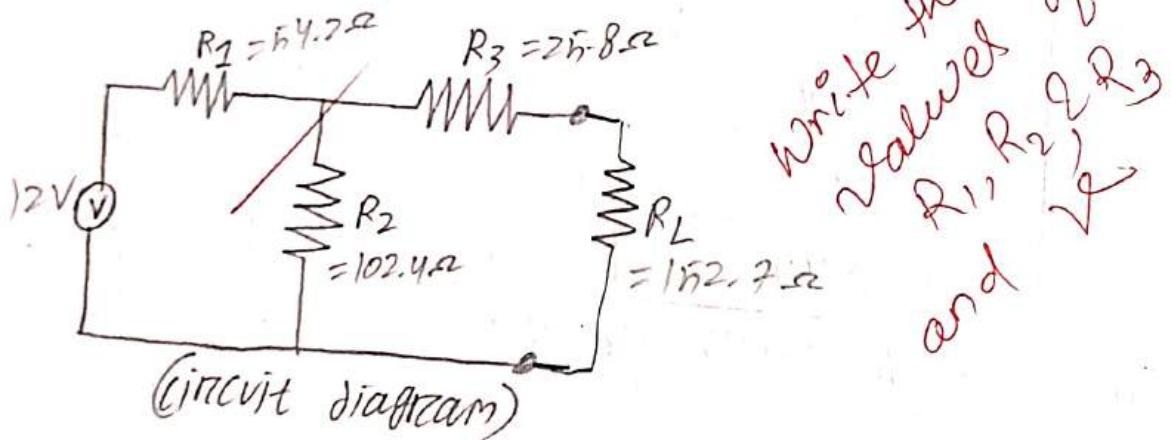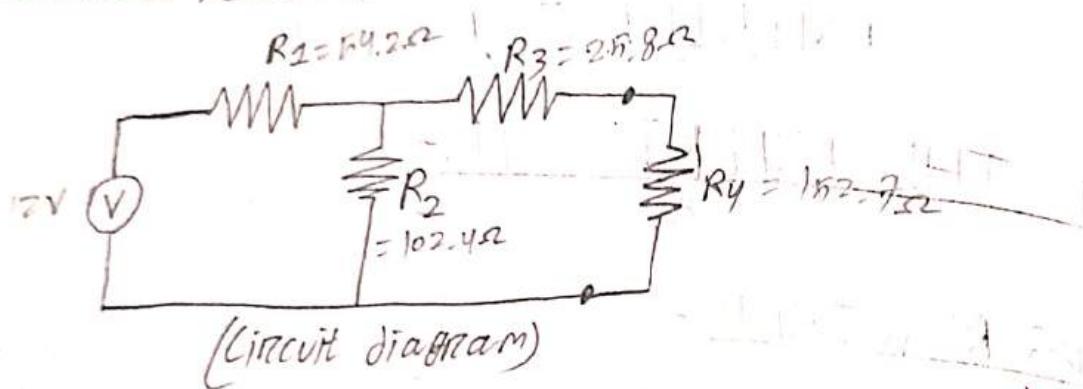

# G. I. E. T. UNIVERSITY

GUNUPUR

2<sup>nd</sup>

SHEET NO. 27

To determine  $R_{th}$ , I proceed as follows:

- I open the voltage source.
- I replace the voltage source with its internal resistance.
- I remove the load resistance.
- I measure the equivalent resistance ( $R_{th}$ ) across the open load terminals.

Once I obtain  $V_{th}$  and  $R_{th}$ , I calculate the load current  $I_L$  using the formula:

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$



## PROCEDURE :-

1. First, I short the 12 V DC terminals (+ and -).
2. I measure the equivalent resistance ( $R_{th}$ ) across  $P_3$  and  $P_4$ .
3. Next, I connect the (-12 V) DC supply to the 12 V DC terminals of the given circuit.
4. I then measure the voltage  $V_{th}$  across the terminals  $P_3$  and  $P_4$ .
5. After that, I ~~short~~ short  $F_4$  and  $L_2$ , then connect an ammeter across  $P_3$  and  $L_1$  in the Thevenin's equivalent circuit.
6. I also place an ammeter across  $P_9$  and  $L_5$  in the general electrical circuit and record the readings.
7. Finally, I compare the ammeter readings of the general electrical circuit and Thevenin's equivalent circuit to confirm the theorem.



SEMESTER \_\_\_\_\_

# G. I. E. T. UNIVERSITY

## GUNUPUR

SHEET No. \_\_\_\_\_

### OBSERVATION:-

Voltage across  $102.4\Omega$  ( $R_2$ ) resistor is

$$= \frac{12 \times 102.4}{54.2 + 102.4}$$

$$V_{R_2} = 7.84V$$

$$R_1 = 54.2\Omega$$

$$R_2 = 102.4\Omega$$

$$R_3 = 25.8\Omega$$

$$R_{th} = (54.2 || 102.4) + 25.8$$
$$= 35.44 + 25.8$$
$$= 61.24\Omega$$

$$I_L = \frac{7.84}{61.24 + 152.7}$$
$$= 0.036A$$
$$= 36mA$$

The value of  $R_1 = 54.2\Omega$ ,  $R_2 = 102.4\Omega$  and  $R_3 = 25.8\Omega$



# G. I. E. T. UNIVERSITY

**GUNUPUR**

SEMESTER \_\_\_\_\_

2<sup>nd</sup>

SHEET No. \_\_\_\_\_


19

## TABULATION:-


SL No.	Practical		Theoretical	
	$I_L$ (mA)	$V_{th}$ (V)	$I_L$ (mA)	$V_{th}$ (V)
1	36.7mA	7.78V	36 mA	7.78V
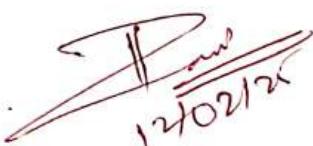
## CONCLUSION :-


The practical values of Thevenin's equivalent voltage and resistance closely match the theoretical calculations, validating Thevenin's theorem. Any slight variations can be attributed to experimental limitations such as measurement errors and component tolerances.




12/02/22

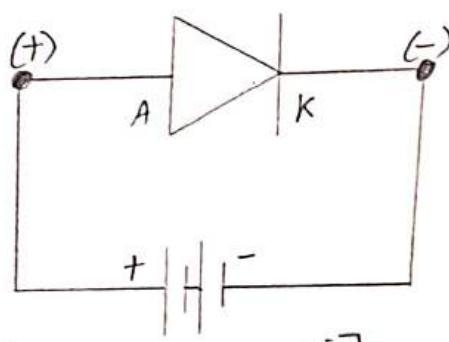


Forward biased connection

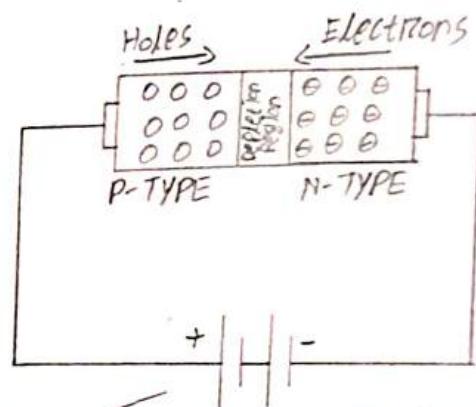

[PN Junction Diode Forward Biasing]

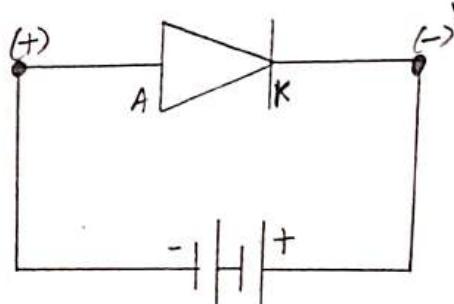

REVERSE biased connection

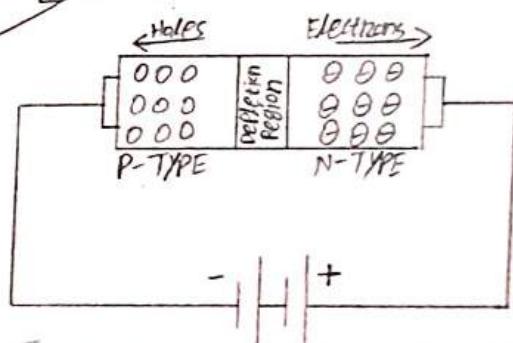

[PN Junction Diode Reverse Biasing]



# G. I. E. T. UNIVERSITY

## GUNUPUR

SEMESTER

2<sup>nd</sup>

SHEET No.

20

### EXPERIMENT NO. :- 05

#### AIM OF THE EXPERIMENT :-

To study the V-I characteristics graph of P-N junction diode.

#### APPARATUS REQUIRED:-

- Patch chords
- V-I characteristics board
- Multi-meter
- Ammeter (mA, MA)

#### OBJECTIVE:-

To Plot graph for forward and reverse biased condition of a P-N junction diode.

#### THEORY:-

Biasing: - The process by which an external DC Voltage is applied to the electric circuit in P-N junction biasing is performed.

Forward Biasing: - The diode is forward biased by connecting the P-side of the positive terminal and the N-side to the negative terminal of the supply voltage. At a particular voltage, the width of the depletion region vanishes and a sharp rise in current and voltage is observed as threshold or knee voltage.

Reverse Biasing: - The diode is reverse biased by connecting the N-side to the positive terminal and the P-side to the negative terminal of the supply voltage. Due to this, more negative ions are generated in the P-side and more positive ions in the N-side, increasing the width of the depletion region. When the applied voltage is increased, the diode enters the breakdown region at a particular point, and this negative voltage is noted as the Peak Inverse Voltage (PIV). The PIV is the maximum reverse voltage applied to a diode before entering the breakdown region.

NAME Rajesh Rana

DATE 25/02/25

UNIV. ROLL \_\_\_\_\_

COLL. ROLL 24KSEAIML015

SCALE :

In X-Axis: 1cm = 0.10 V

In Y-Axis: 1cm = 1 mA

In X'-Axis: 1cm = 2 V

In Y'-Axis: 1cm = 0.10 mA

X

10

9

8

7

6

5

4

3

2

1

0.10

0.20

0.30

0.40

0.50

0.60

0.70

0.80

0.90

1.0

Y

Scaling?

0

0

0

0

0

0

0

X

-16 -14 -12 -10 -8 -6 -4 -2 0

0.10

0.20

0.30

0.40

0.50

0.60

0.70

0.80

0.90

1.00

1.2

1.4

1.6

1.8

2.0

2.2

2.4

2.6

2.8

3.0



# G. I. E. T. UNIVERSITY

## GUNUPUR

SEMESTER

2<sup>nd</sup>

SHEET No.

21

### PROCEDURE :-

#### For Forward Biased :-

- The circuit is connected so that the positive side of the external DC source is connected to the P-side of the diode and the negative side to the N-side.
- An ammeter and a multimeter are connected to the diode.  
The ammeter used is a milliamperere ammeter.
- The DC voltage is varied in steps up to 8V (up to knee voltage), and the corresponding ammeter readings are noted.

#### For Reverse Biased :-

- The positive side of the external DC source is connected to the N-side, and the negative side is connected to the P-side of the diode.
- The applied voltage is varied up to the breakdown voltage.
- The corresponding ammeter readings are noted.

### OBSERVATIONS:-

#### Forward Biased :-

SL. NO.	Voltage (V) in Volt	Current (I) in mA
1	0.16	0
2	0.25	0
3	0.39	0
4	0.47	0.2
5	0.53	0.7
6	0.54	0.8
7	0.56	1.2
8	0.58	2.0
9	0.59	2.5
10	0.60	3.2
11	0.62	4.4

UNIV. ROLL \_\_\_\_\_

NAME Rajesh Rana

75162125



SEMESTER

# G. I. E. T. UNIVERSITY

## GUNUPUR

2<sup>nd</sup>

SHEET No.

22

12	0.64	6.3
13	0.65	7.9
14	0.66	9.0
15	0.67	11.7

Reverse Biased :-


SL. NO.	VOLTAGE (V) IN VOLT	CURRENT (I) IN MA
1	0.5	0
2	1.1	0.1
3	1.8	0.2
4	2.6	0.3
5	3.4	0.4
6	4.10	0.5
7	5.0	0.6
8	5.8	0.7
9	6.9	0.8
10	8.5	0.9
11	9.0	1.0
12	10.0	1.1
13	10.8	1.2
14	11.4	1.3
15	12.4	1.4

CONCLUSION :-

The V-I characteristics of a P-N junction diode in both forward and reverse bias are successfully studied.

Sandeep  
AT3125

INPUT SIGNAL

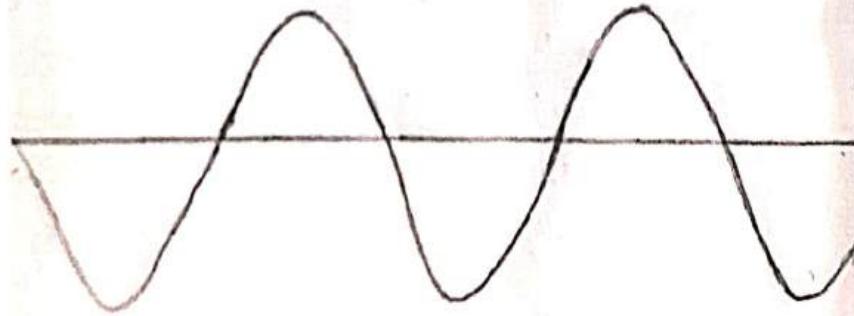

Amplitude = 9V



# G. I. T. UNIVERSITY

GUNUPUR

2<sup>nd</sup>

SHEET No.

23

## EXPERIMENT NO:- 06

### Aim Of The Experiment :-

To study about the half-wave & full-wave rectifier circuits with and without capacitor filters and recording the output waveforms.

### Objective :-

- > To trace the input and rectified output waveforms.
- > Measurements of average and root mean square values of the rectifier output.

### Components Required :-

- > Rectifier trainer kit
- > CRO
- > CRO Probe
- > Voltmeter
- > Connective wire

### Theory :-

Semiconductor diode is a simple combination of P-type and N-type material. It is formed by doping half of the silicon crystal with trivalent impurity (P-type) and the half with pentavalent material (N-type). It has the characteristics of passing.

Rectifier :- It is a device which converts AC voltage to pulsating DC voltage using one on one diode. It is two types :- one is half wave rectifier and second is full wave rectifier. The conventional currents flow through D, load resistor ( $R_L$ ) and upper half of the secondary winding, similarly during -ve half cycle.

UNIV. ROLL \_\_\_\_\_


NAME Ravish Rana

04/03/25

HALF WAVE



Amplitude - 8V

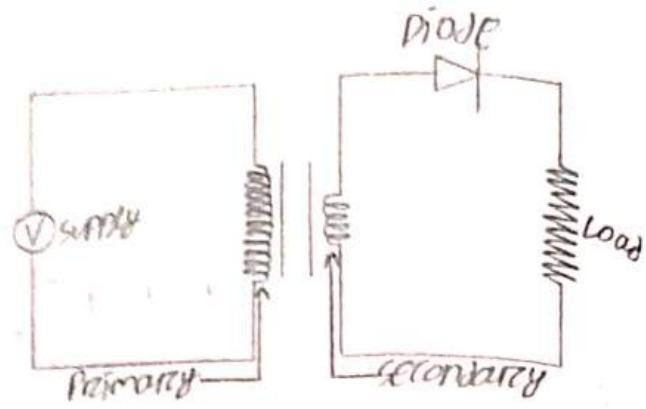


[Half wave Rectifier]

FULL WAVE




Amplitude - 8V

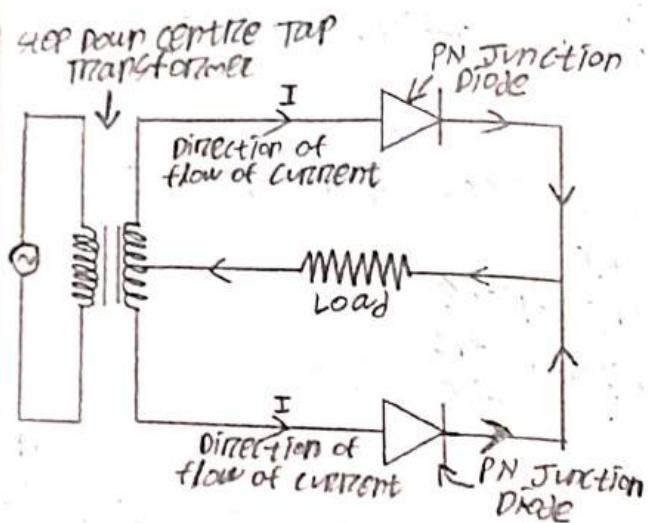


[Full wave Rectifier]

BRIDGE WAVE

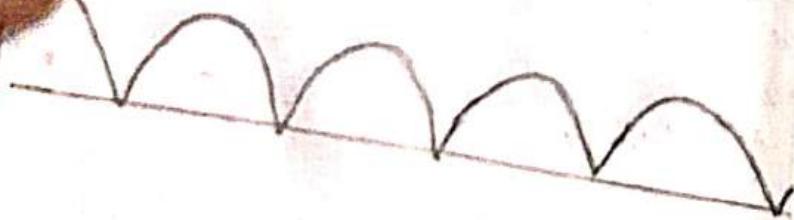

Amplitude - 7V

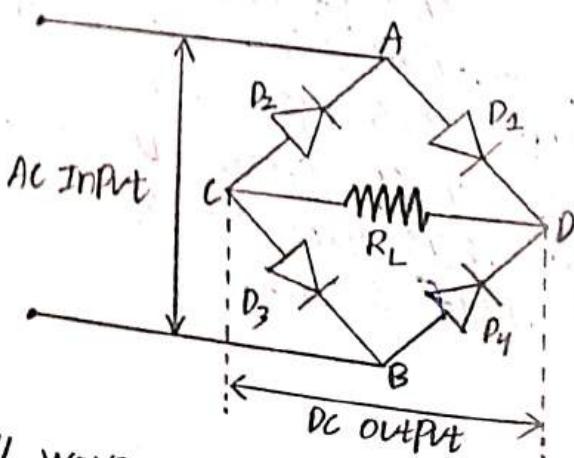

[Full wave Bridge Rectifier]



SEMESTER

# G. I. E. T. UNIVERSITY

## GUNUPUR

2<sup>n</sup>

SHEET No.

24

### Half wave rectifier:-

- The rectifier conducts current only during the positive half cycle of input AC supply, in which the diode is forward biased.

$$V_o = I \cdot R_L$$

- For negative half cycle of AC input supply no current flows and so no voltage appears across the load as diode is reverse biased and hence open circuit.

$$V_o = 0V$$

- The transformer allows to step up/step down the AC input voltage and also isolates the rectifier circuit from line and thus reduces the risk of electric shocks.
- The AC supplier delivers power only on the time i.e. output is low.

### Full wave rectifier:-

- In the positive half cycle, A becomes positive and B becomes negative. This makes D<sub>1</sub> forward bias, D<sub>2</sub> reverse bias and open circuit. Hence D<sub>1</sub> conducts current while D<sub>2</sub> does not.
- The conventional current flows through D<sub>1</sub>, load resistor (R<sub>L</sub>) and upper half of the secondary winding.
- Similarly, during -ve half cycle end A becomes -ve and B is +ve and D<sub>2</sub> is reverse and D<sub>1</sub> is forward bias. Hence, current flows through D<sub>2</sub>, R<sub>L</sub> and lower half of winding.

### Full wave bridge rectifier :-

- Here +ve diodes are used without using center tapped transformer.
- The AC supply to be rectified is applied to the diagonally end of the bridge through transformer.
- During the +ve half cycle of the voltage and if A becomes +ve and B becomes -ve then D<sub>2</sub> and D<sub>3</sub> is forward bias. These two diode will be the forward biased. These two diode will be the series through the load (R<sub>L</sub>). Hence DC supply output is obtained across R<sub>L</sub>.

UNIV. ROLL \_\_\_\_\_

NAME Ravjesh Rana

2019 ATMI 015

2011-12-1-



# G. I. E. T. UNIVERSITY

## GUNUPUR

2<sup>nd</sup>

SEMESTER

SHEET NO.

25

In -ve half cycle  $D_2$ ,  $D_3$  are reversed biased while  $D_1$  and  $D_4$  are forward biased. So, current conductive through  $D_1$ ,  $D_4$  and  $R_L$ . Hence output across it each case (P/V) of each diode is  $V_m$ .

### PROCEDURE :-

- First configure the half wave rectifier circuit as shown in the circuit diagram.
- I noted the values of all components and connected the primary side of the transformer to the AC main supply while the secondary side was connected to the input circuit.
- I measured the DC and AC voltage and current values both with and without load.
- I repeated the process with an 'L' and 'pi' filter to observe variations in the DC and AC Voltage and current values.
- I followed the same procedure of the full-wave rectifier and the full-wave bridge rectifier circuits.

### OBSERVATION AND CALCULATION TABLE :-


SL. NO.	TYPES OF RECTIFIER	INPUT VOLTAGE(V)	RECTIFIED OUT VOLTAGE(V)
1	Half wave	9V	8V
2	Full wave	9V	8V
3	Full wave bridge	9V	7V

### CONCLUSION :-

This experiment confirmed that half-wave rectifiers allow conduction only during the positive half-cycle, while full-wave rectifiers provide continuous pulsating DC output. The bridge rectifier improves efficiency without requiring a center-tapped transformer.

S. H. Aw  
11/03/25

## CIRCUIT DIAGRAM:-

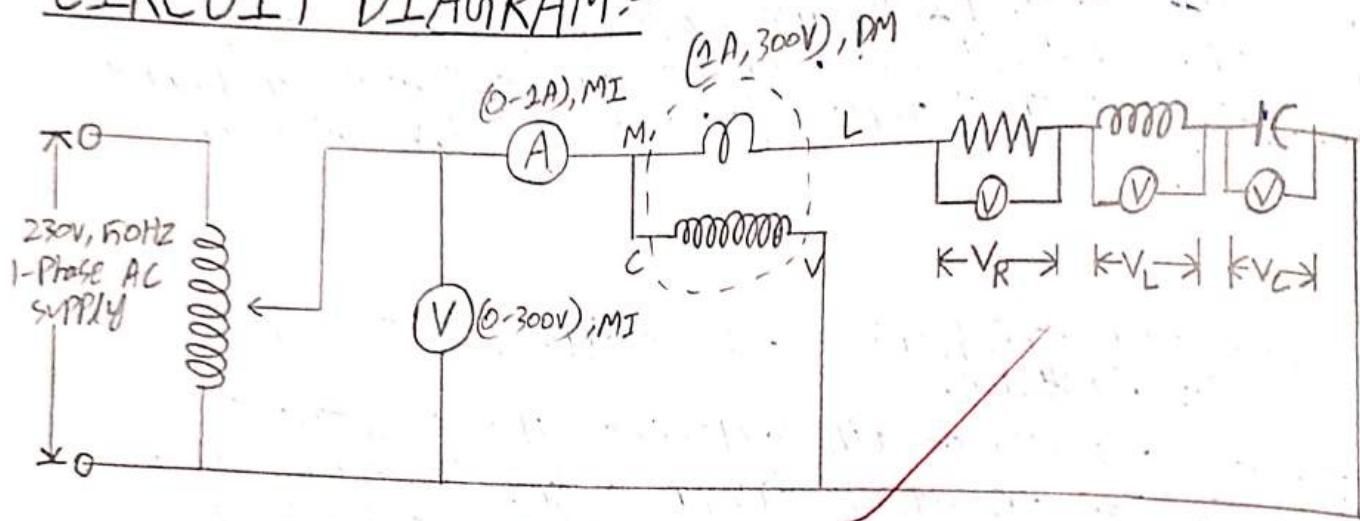



SEMESTER

# G. I. E. T. UNIVERSITY

**GUNUPUR**

2<sup>nd</sup>

SHEET NO. 26

## EXPERIMENT NO:- 07

### AIM OF THE EXPERIMENT :-

Measurement of current voltage power factor in series R-L-C circuit excited by a single phase AC supply.

### APPARATUS REQUIRED :-

SL. NO.	COMPONENTS	RATING	TYPE	QUANTITY
1	Voltmeter	0-300V	MI	1
2	Ammeter	0-1A	MI	1
3	Wattmeter	1A, 300V	DM	1
4	Bulb	230V, 40W	RESISTIVE	1
5	Choke	230V, 40W	INDUCTIVE	1
6	Capacitor	230V, 0.25μF	Electrolytic	1
7	Variac	0-230-270V, 8A	WW	1
8	Connecting wires	230V, 6A, 1/18SWG	PVC Coated	AS PER REQUIRED

### THEORY :-

Power in an electrical circuit can be measured using a wattmeter. A wattmeter consists of two coils, namely current coil and pressure coil or potential coil. The current coil is marked as ML and pressure coil is marked as a CV. The current coil measures the quantity that is proportional to the current in the circuit. The pressure coil measures quantity that is proportional to the voltage in the circuit. The given wattmeter is loaded by direct loading. The ammeter is connected in series to the wattmeter. Since the same current flows in both the coils, the current and voltage across the circuit are constant. The power consumed by the load is measured using the wattmeter.

UNIV. ROLL \_\_\_\_\_

NAME Ravish RahaCOLL. ROLL 2UCSEAIML015DATE 11/03/25



SEMESTER

# G. I. E. T. UNIVERSITY

## GUNUPUR

2<sup>nd</sup>

SHEET No. 27

and calculated using the relation given below.

A series RLC circuit with Kirchoff's voltage law given:

$$V = \sqrt{R^2 + V_L^2 + V_C^2}$$

$$= I(R + j\omega L + 1/j\omega C)$$

$$= \boxed{I} Z$$

In the above circuit, one can say whether current leads or lags the voltage. It depends upon relative value of terms  $\omega L$  &  ~~$1/\omega C$~~ .

There can be three possibilities

If  $\omega L > 1/\omega C$ , the current leads the voltage and circuit behaves as inductive circuit.

If  $\omega L < 1/\omega C$ , the current lags the voltage and circuit behaves as capacitive circuit.

Special case: At resonance the current through the circuit becomes in phase with supply voltage.

### PROCEDURE :-

- I connect the circuit as shown in the circuit diagram.
- Initially, I ensure that no load is applied.
- Before switching on the power supply, I set the auto transformer to its minimum voltage position.
- I set the rated voltage using the auto transformer and measure the voltmeter, ammeter, and wattmeter readings under no-load conditions. I also carefully note the multiplication factor mentioned on the wattmeter.
- I apply the load by adjusting the RLC load.
- I measure and record the values of the voltmeter, ammeter and wattmeter.
- I repeat steps 5 and 6 until the ammeter reading reaches 10A.
- After taking all the readings, I slowly reduce the load to the minimum and bring the voltage to the lowest setting on the auto transformer. Then, I switch off the power supply.
- I calculate the indicated power using the given formula.
- I determine the power factor using the given formula.



# G. I. E. T. UNIVERSITY

GUNUPUR

SHEET No. 28

2<sup>nd</sup>

## FORMULA:-

Actual Power =  $W * \text{multiplication factor}$ .  
where,  $W$  = observed wattmeter reading

Apparent Power =  $VI$

where,  $V$  = Voltmeter reading

$I$  = Ammeter reading

Power factor,  $\cos\phi$  = Actual Power/Apparent Power.

## OBSERVATION:-

Sl. No.	Voltage V (Volt)	Current I (AMP)	Wattmeter Reading(Watt)		Measured Power (VA)	Power factor ( $\cos\phi$ )	Mean
			Observed	Actual			
1	140 V	0.20 A	15.9	23.6	28	0.84	
2	160 V	0.21 A	7.2	28.8	33.6	0.85	
3	180 V	0.22 A	8.7	34.8	39.6	0.87	0.868
4	200 V	0.23 A	10.2	40.8	46	0.88	
5	220 V	0.24 A	11.9	47.6	52.8	0.90	

## CONCLUSION:-

This experiment verified the measurement of current, voltage and power factor in a series RLC circuit. The results confirmed theoretical phase relationships and the dependence of power factor on circuit parameters.

*H. Panigrahi*  
18/103/26



# G. I. E. T. UNIVERSITY

GUNUPUR

SEMESTER

2<sup>nd</sup>

SHEET NO.

79

## EXPERIMENT NO :- 28

Aim of the experiment :-

Power factor measurement for fluorescent lamp.

Apparatus Required:-

SL NO	Name of the Equipment	Range	Type	Quantity
1	Fluorescent lamp	230V, 20W	TUBE	1
2	Voltmeter	0-1 A	MI	1
3	Ammeter	230 V, 20W	MI	1
4	choke coil	230 V, 20W	Inductive	1
5	starter	230 V, 20W	Glow type	1
6	Capacitor	2.5 μF	oil filled	1
7	wattmeter	1A, 300Y	DM	1
8	connecting wires	230V FA 1/18 SWG	PVC Coated	As per required
9	Variac	0-270V, 8A	WW	1

Theory :-


A fluorescent lamp is a low pressure mercury discharge lamp with inner surface coated with suitable fluorescent materials. This consists of glass tube provided at both ends with caps having two pins an oxide coated tungsten filament tube contains argon or krypton gas to facilitate starting with small quantity of mercury under low pressure. Fluorescent material when subjected to electromagnetic radiations of particular wavelength produced by the discharge through the mercury vapor get excited and in turn gives out radiations at some other wavelength which falls under visible spectrum. Power factor of the lamp is somewhat low and is about 0.5 lagging due to induction of the choke. A condenser, if connected across the supply improves the power factor. When rated supply applied, full supply voltage appears across starter electrode & cathode which are enclosed in a glass

UNIV. ROLL \_\_\_\_\_

NAME \_\_\_\_\_ Rajesh Rana

COLL. ROLL 24/CSEAIML015

DATE 18/03/25

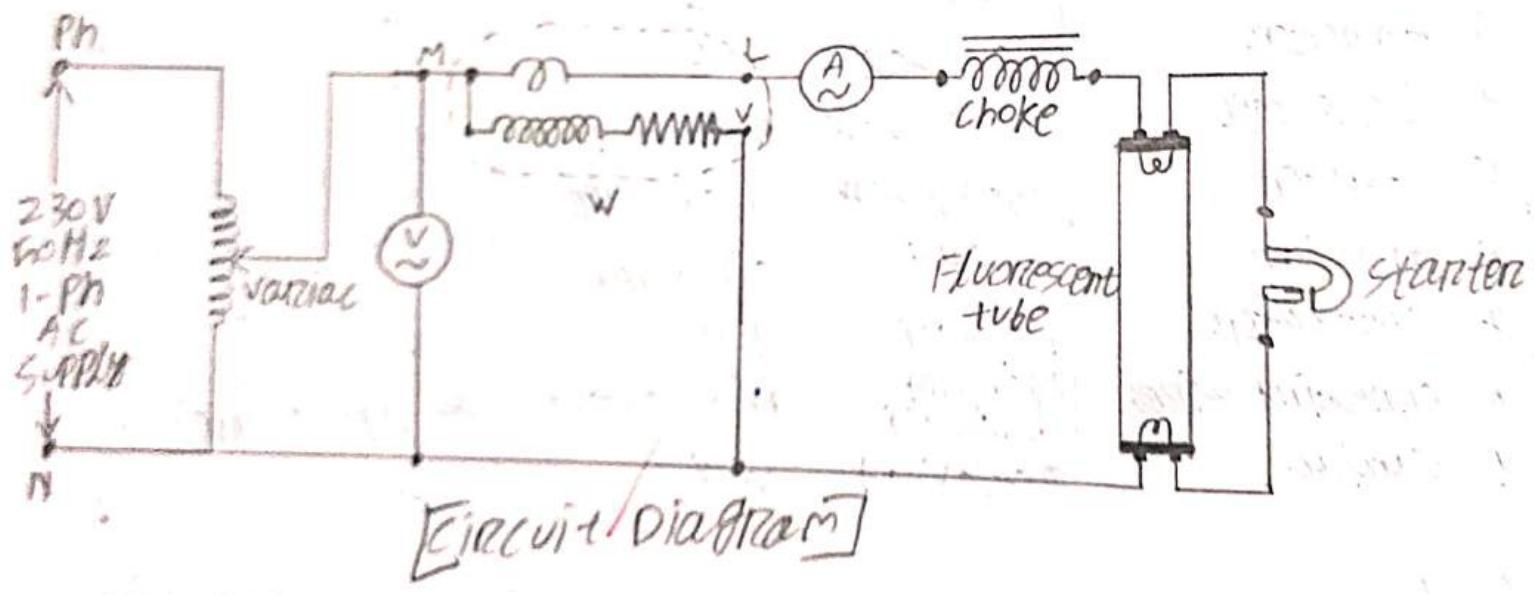



# G. I. E. T. UNIVERSITY

GUNUPUR

SEMESTER

2<sup>nd</sup>

SHEET NO.

30

Tube filled with argon gas. This voltage causes discharge in the tube, the electrodes P which is made of bimetallic strip, bends and closes contact of the starter. At this stage, the choke the filament M<sub>1</sub> and M<sub>2</sub>, of the tube T and the starter becomes connected in series across the supply. A current flows through filament M<sub>1</sub> and M<sub>2</sub> and heats them. Meanwhile the argon discharge in the starter tube, the electrodes P and causes a sudden break in the circuit. This causes a high value of induced emf in the choke. The induced emf in the choke is applied across tube light electrodes M<sub>1</sub> and M<sub>2</sub> and is responsible for initiating a gaseous discharge because initial heating has already created good number of free electrons in the vicinity of electrodes. Thus the starts giving light output. Once the discharge through the tube light is established, a lower voltage than supply voltage is required to maintain. A reduction during running condition is achieved by having voltage drop in the choke.

The capacitor connected between the starter terminals P and Q is used to suppress the electromagnetic waves generated at the gap due to sparking, thereby reducing the disturbance caused to nearby radio and tv receivers.

Procedure:-

I connected the circuit, switched on the supply, and slowly increased the voltage to the rated level. I noted the voltage, current, and power readings and calculated the power factor.

Calculation:-

$$\text{Actual Power} = \text{observed power} \times \text{M.F.(Y)}$$

$$\text{Power factor} = \cos \phi = \frac{\text{Actual Power}}{V \times I}$$

$$\cos \phi = \frac{\text{Actual Power}}{V \times I}$$

UNIV. ROLL \_\_\_\_\_

NAME Ravish Raha

COLL. ROLL 24CSEAI1MLO15

DATE 18/03/25



SEMESTER

# G. I. E. T. UNIVERSITY

GUNUPUR

2nd

SHEET No.

31

Observation Table:-


Sl. No.	voltmeter reading in Volts	Ammeter reading in Amperes	wattmeter reading In watt		power factor = $\cos \phi$	mean
			observed	Actual		
1	220	0.42	9.6	38.4	0.41	
2	210	0.38	8.7	34.8	0.43	
3	200	0.36	7.9	31.8	0.44	0.442
4	190	0.33	7.2	28.8	0.45	
5	180	0.30	6.5	26	0.48	

Conclusion :-


In this experiment, I successfully connected in the circuit, measured voltage, current and power and calculated the power factor. The results help in understanding the circuit's efficiency and performance.

  
25/03/20

### OR Gate:-

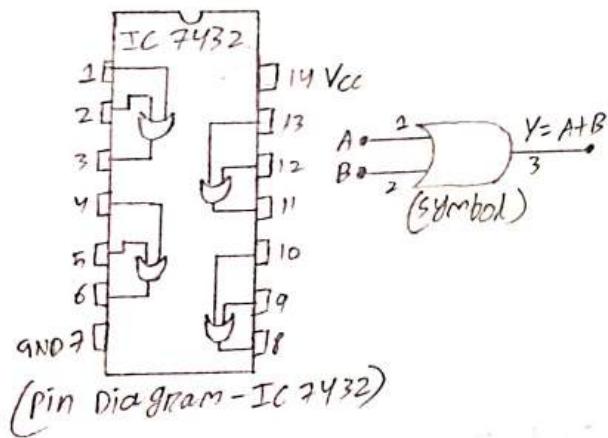

### AND Gate:-

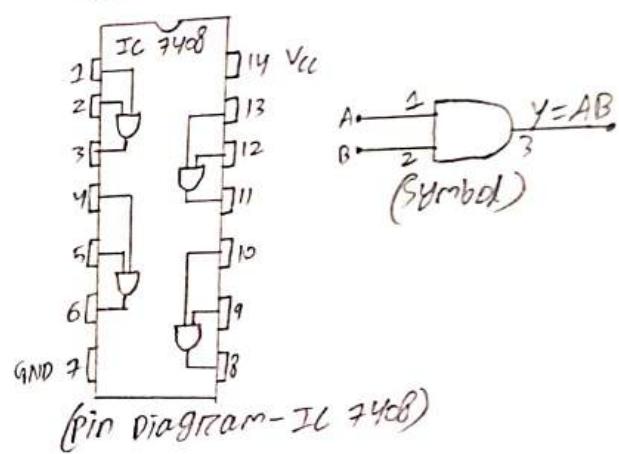



SEMESTER

# G. I. E. T. UNIVERSITY

**GUNUPUR**

2nd

SHEET No. 32

EXPERIMENT NO:-01

Aim Of The Experiment :-  
To study and verify different logic gates.

Objective :-

To familiarize with circuit implementations using ICs and test the behaviour of different logic gates.

Components Required :-

- Digital bread board / Project board
- Connecting Patch chords
- IC 7400, IC 7408, IC 7432, IC 7402, IC 7404, IC 7486

Theory :-

The basic logic gates are the building blocks of more complex logic circuits. These logic gates perform the basic Boolean function such as AND, OR, NAND, NOR, Inversion, Exclusive OR and Exclusive NOR.


These basic logic gates are implemented as small scale integrated circuits (IC) or as part of more complex medium scale (MSI) or very large scale (VLSI) integrated circuits. Digital IC Gates are classified not only by their logic operation but also the specific logic-circuit family to which they belong. Each family has its own basic electronic circuit upon which more complex digital circuits and functions are developed.

Gate	Description	Truth Table															
OR	The output is active high if any one of the inputs is in active high state. mathematically, $Q = A + B$	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>Output</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>0</td></tr> <tr> <td>0</td><td>1</td><td>1</td></tr> <tr> <td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	Output	0	0	0	0	1	1	1	0	1	1	1	1
A	B	Output															
0	0	0															
0	1	1															
1	0	1															
1	1	1															
AND	The output is active high only if both the inputs are in active high state. mathematically, $Q = A \cdot B$	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>Output</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>0</td></tr> <tr> <td>0</td><td>1</td><td>0</td></tr> <tr> <td>1</td><td>0</td><td>0</td></tr> <tr> <td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	Output	0	0	0	0	1	0	1	0	0	1	1	1
A	B	Output															
0	0	0															
0	1	0															
1	0	0															
1	1	1															


UNIV. ROLL \_\_\_\_\_

NAME Rajesh RanuCOLL. ROLL 24CSEAIML025DATE 08/04/25


### NOR Gate:-

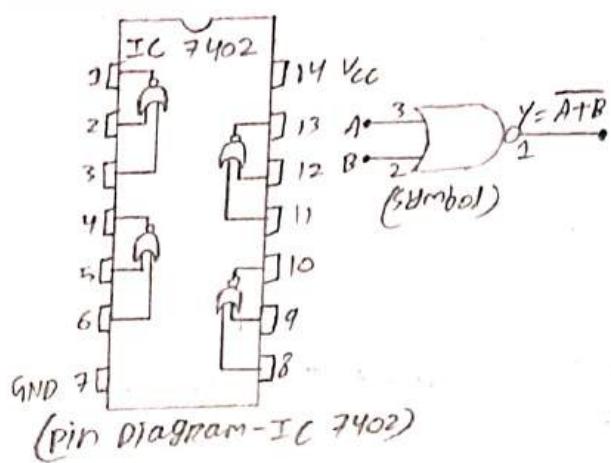


### NAND Gate:-

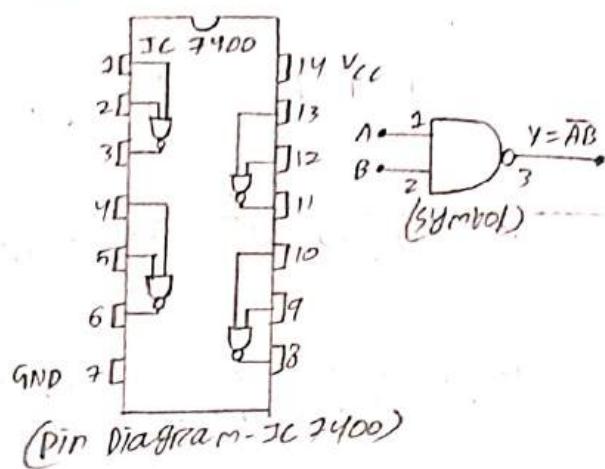

### NOT Gate:-

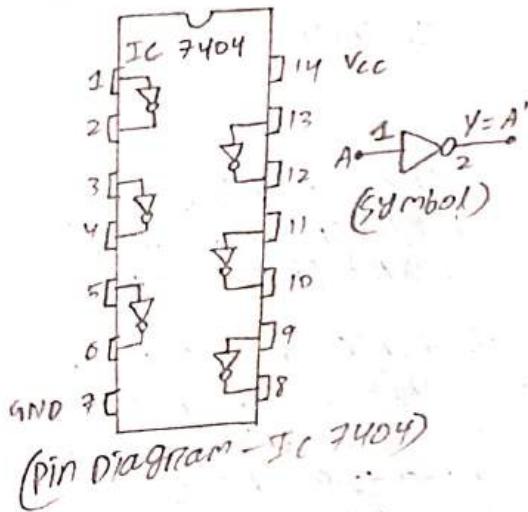

### X-OR gate:-

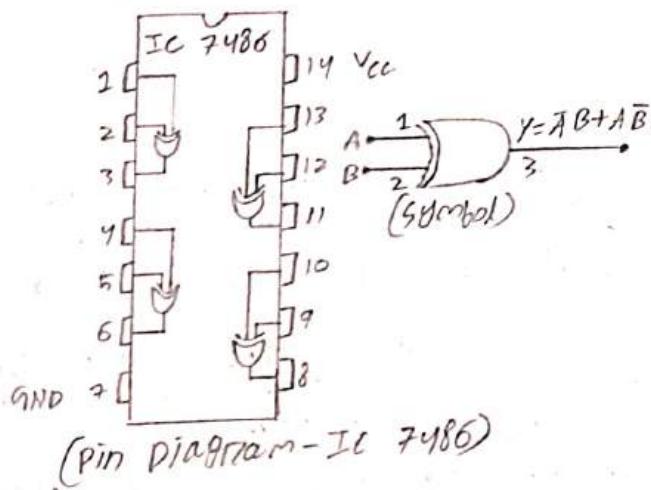



SEMESTER

# G. I. E. T. UNIVERSITY

## GUNUPUR

2<sup>nd</sup>

SHEET No.

33

Gate	Description	Truth Table															
NOR	The output is active high only if both the inputs are in active low state. Mathematically, $Q = (A+B)'$	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>Output</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Output	0	0	1	0	1	0	1	0	0	1	1	0
A	B	Output															
0	0	1															
0	1	0															
1	0	0															
1	1	0															
NAND	The output is active high only if any one of the inputs is in active low state. Mathematically, $Q = (A \cdot B)'$	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>Output</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Output	0	0	1	0	1	1	1	0	1	1	1	0
A	B	Output															
0	0	1															
0	1	1															
1	0	1															
1	1	0															
NOT	In this gate the output is opposite to the input state. Mathematically, $Q = A'$	<table border="1"> <thead> <tr> <th>A</th><th>Output</th></tr> </thead> <tbody> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </tbody> </table>	A	Output	0	1	1	0									
A	Output																
0	1																
1	0																
XOR	The output is active high only if any one of the input is in active high state. Mathematically, $Q = A'B + AB'$	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>Output</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Output	0	0	0	0	1	1	1	0	1	1	1	0
A	B	Output															
0	0	0															
0	1	1															
1	0	1															
1	1	0															

Conclusion:-

The experiment successfully demonstrated the working of basic logic gates including AND, OR, NOT, NAND, NOR and XOR using digital ICs. The observed outputs matched the expected truth tables, verifying the correct operation of each gate. This practical exercise enhanced our understanding of digital logic fundamentals and circuit behaviour.