


UNIT-11

SINGLE - PHASE AC Circuits

18

AC Fundamentals

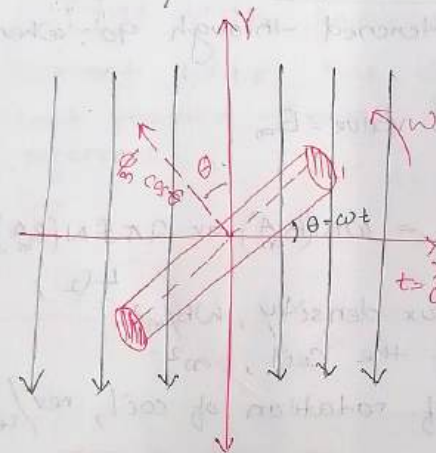Alternating voltage may be generated by rotating a coil in a magnetic field or by rotating a magnetic field within a stationary coil.



Consider a rectangular coil having N turns & rotating in a uniform magnetic field, with an angular velocity of ω rad/sec

[Ang. velocity :-

Let time (t) \rightarrow x -axis.

$\phi_m \rightarrow$ Max. flux w.r.t x -axis.

In time- t Sec, this coil rotates through an angle $\theta = \omega t$. On this deflected position, the component of the flux which is \perp to the plane of coil is

$$\phi = \phi_m \cos \omega t$$

Hence flux linkages of coil at any time are $N\phi = N\phi_m \cos \omega t$

According to Faraday's laws of Electro-magnetic induction, the emf induced in the coil is given by the rate of change of flux-linkages of coil. Hence, the value of induced emf at this instant i.e. $\theta = \omega t$

or instantaneous value of the emf is

$$\begin{aligned} e &= -\frac{d}{dt}(N\phi) = -N \frac{d}{dt}(\phi_m \cos \omega t) \\ &= -N\phi_m \omega (-\sin \omega t) \\ e &= \omega N \phi_m \sin \omega t \text{ volt} \\ &= \omega N \phi_m \sin \theta \quad \text{--- (1)} \end{aligned}$$

When coil has turned through 90° : when $\theta = 90^\circ$ then $\sin \theta = 1$.

so e has max. value $= E_m$.

eqⁿ (1) become

$$E_m = \omega N \phi_m = \omega N(B_m A) \text{ or } 2\pi f N(B_m A) \quad \text{--- (2)}$$

$B_m \rightarrow$ Max. flux density, Wb/m^2

$A \rightarrow$ area of the coil, m^2

$f \rightarrow$ freq of rotation of coil, rev/sec

By putting eqⁿ (2) in (1)

$$e = E_m \sin \theta = E_m \sin \omega t \quad \text{--- (3)}$$

$$\text{||}^{\text{ty}} \quad i = I_m \sin \omega t \quad \text{--- (4)}$$

eqⁿ of induced alternating current.

Some Common terms \Rightarrow

a) Cycle :- One Complete set of +ve & -ve values of alternating quantity is known as Cycle.

\rightarrow One Complete cycle $= 360^\circ$ or 2π radians.



b) Time-period \Rightarrow The time-taken by an alternating quantity to complete one cycle is time-period (T).

c) Frequency \Rightarrow The number of cycles/sec 19 is called the freq. of unit = Hertz (Hz).

$$\boxed{f = \frac{1}{T}} \text{ or } \boxed{T = \frac{1}{f}}$$


d) Amplitude \Rightarrow The max. value, +ve or -ve of an alternating qty is known as its amplitude.

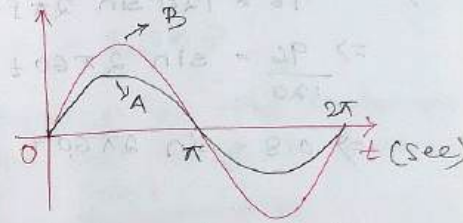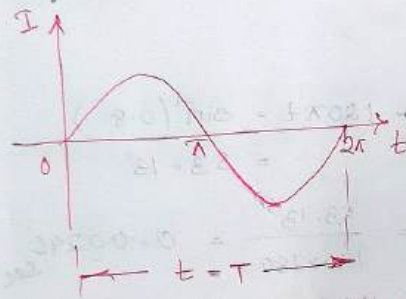e) Phase \Rightarrow The fraction of T of that alternating current which has elapsed since the current last passed through the zero position of reference.



[A & B are in same phase]

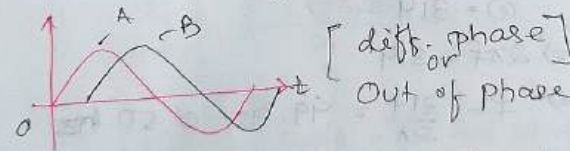f) Phase difference \Rightarrow "The angular phase diff. betⁿ the max. possible value of the 2 alternating quantities having same freq".



[diff. phase]
Out of phase

1) An alternating current of freq 60 Hz has a max. value of 120 A. Write down the eqⁿ for its instantaneous value. Reckoning time from the instant the current is zero & is becoming +ve. Find a) instantaneous value after $\frac{1}{360}$ sec (b) time taken to reach 96 A for the 1st time.

$$50)^n \quad f = 60 \text{ Hz}$$

$$\omega = 2\pi f = 2\pi \times 60 = 377.1$$

Instantaneous current eqⁿ is

$$i = I_m \sin \omega t$$

$$= 120 \sin 120\pi t$$

a) when $t = \frac{1}{360} \text{ s}$ then

$$i = 120 \sin \left(120\pi \times \frac{1}{360} \right) = 120 \sin \left(\frac{\pi}{3} \right)$$

$$= \underline{103.9 \text{ A}} \quad (\text{in rad})$$

$$b) \quad 96 = 120 \sin 2\pi f t$$

$$\Rightarrow \frac{96}{120} = \sin 2\pi 60 t$$

$$\Rightarrow 0.8 = \sin 2\pi 60 t \Rightarrow 120\pi t = \sin^{-1}(0.8) \\ = 53.13^\circ$$

$$t = \frac{53.13}{120\pi} = \frac{53.13}{120 \times 180} = 0.00246 \text{ sec}$$

2) An ac is given by $i = 141.4 \sin 314t$, find out max. value, freq. & time period.

$$i = 141.4 \sin 314t$$

$$\Rightarrow i = I_m \sin \omega t$$

$$I_m = 141.4 \text{ A}, \quad \omega = 314$$

$$\Rightarrow 2\pi f = 314$$

$$\Rightarrow f = \frac{314}{2\pi} = 49.95 \approx 50 \text{ Hz}$$

$$T = \frac{1}{f} = \underline{0.02 \text{ sec}}$$

Root-Mean-Square (RMS) Value:-

20

The rms value of an alternating current is given by "steady (dc) current which when flowing through a given circuit for a given time produces the same heat as produced by AC when flowing through the same circuit for the same time."

↳ It's also known as the effective or virtual value of alternating current.

Mathematical expression:-

The standard form of a sinusoidal alternating current is

$$i = I_m \sin \omega t = I_m \sin \theta$$

The mean of the squares of the instantaneous values of current over one complete cycle is

$$i.e. \quad I_{rms}^2 = \frac{\int_0^{2\pi} i^2 d\theta}{\int_0^{2\pi} d\theta} = \frac{\int_0^{2\pi} I_m^2 \sin^2 \theta d\theta}{2\pi}$$

$$\text{Square root or } I_{rms} = \sqrt{\int_0^{2\pi} \frac{I_m^2 \sin^2 \theta}{2\pi} d\theta}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \int_0^{2\pi} \sin^2 \theta d\theta}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \int_0^{2\pi} \left(\frac{1 - \cos 2\theta}{2} \right) d\theta}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \left[\int_0^{2\pi} 1 d\theta - \int_0^{2\pi} \cos 2\theta d\theta \right]}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \left[\theta \Big|_0^{2\pi} - \frac{\sin 2\theta}{2} \Big|_0^{2\pi} \right]}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \left[(2\pi - 0) - \frac{1}{2} (\sin 4\pi - \sin 0) \right]}$$

$$= \sqrt{\frac{I_m^2}{4\pi} [2\pi]} = \sqrt{\frac{I_m^2}{2}} \Rightarrow \boxed{I_{rms} = \frac{I_m}{\sqrt{2}} = 0.707 I_m}$$

RMS value of a Complex wave \Rightarrow

The rms value of a complex wave is equal to the square root of the sum of the squares of the rms value of its individual elements.

for eg.

$$i = 12 \sin \omega t + 6 \sin \left(3\omega t - \frac{\pi}{6} \right) + 4 \sin \left(5\omega t + \frac{\pi}{8} \right)$$

$$I_{rms} = \sqrt{\left(\frac{12}{\sqrt{2}} \right)^2 + \left(\frac{6}{\sqrt{2}} \right)^2 + \left(\frac{4}{\sqrt{2}} \right)^2}$$
$$= 9.74 \text{ A}$$

Average value $\Rightarrow I_{avg}$

"that steady current which transfers across any circuit the same charge as is transferred by that AC during same time."

$$I_{avg} = \frac{i_1 + i_2 + \dots + i_n}{n}$$

or

$$I_{avg} = \int_0^\pi \frac{i \, d\theta}{\pi}$$

$$= \int_0^\pi \frac{I_m \sin \theta}{\pi} \, d\theta$$

$$= \frac{I_m}{\pi} \left[-\cos \theta \right]_0^\pi = \frac{I_m}{\pi} \left[-\cos \pi + \cos 0 \right]$$

$$= \frac{I_m}{\pi} (1 + 1) = \frac{2I_m}{\pi}$$

$$I_{avg} = \frac{2I_m}{\pi} \quad \text{or} \quad \frac{I_m}{\left(\frac{\pi}{2} \right)} = \underline{\underline{0.637 I_m}}$$

1) An alternating current varying sinusoidally with a freq. of 50 Hz has an rms value of 20 A. Write down the eqⁿ for the instantaneous value & find this value (a) 0.0025 sec (b) 0.0125 sec after passing through a positive max. value. At what time, measured from a +ve max. value, will the instantaneous current be 14.14 A?

$$I_{rms} = 20 \text{ A} ; f = 50 \text{ Hz}$$

$$\Rightarrow I_m = \sqrt{2} I_{rms} = 28.2 \text{ A} = 2\pi f = 100\pi \text{ rad/s}$$

$$i = I_m \sin \omega t$$

$$= 28.2 \sin 100\pi t \text{ A}$$

a) when $t = 0.0025 \text{ s}$

$$i = 28.2 \sin [100\pi \times 0.0025]$$

$$= 28.2$$

$$= 19.94 \approx 20 \text{ A}$$

ii) when $t = 0.0125 \text{ s}$

$$i = 28.2 \sin (100\pi \times 0.0125) = -19.94 \approx -20 \text{ A}$$

iii) when $i = 14.14 \text{ A}$

$$14.14 = 28.2 \sin (100\pi t) \Rightarrow 0.5 = \sin (100\pi t)$$

$$\Rightarrow 100\pi t = 30^\circ$$

$$t = \frac{30}{100\pi}$$

$$= \frac{1}{300} \text{ s}$$

RMS Value of half-wave rectified AC current

↳ One half-cycle has been suppressed.

$$I_{rms} = \sqrt{\frac{\int_0^{2\pi} i^2 d\theta}{2\pi}}$$

$$= \sqrt{\frac{\int_0^{\pi} I_m^2 \sin^2 \theta d\theta}{2\pi}}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \int_0^{\pi} (1 - \cos 2\theta) d\theta}$$



$$\begin{aligned}
 &= \sqrt{\frac{I_m^2}{4\pi} \left[\int_0^\pi 1 \cdot d\theta - \int_0^\pi \cos 2\theta d\theta \right]} \\
 &= \sqrt{\frac{I_m^2}{4\pi} \left[(\pi - 0) - \frac{\sin 2\theta}{2} \Big|_0^\pi \right]} \\
 &= \sqrt{\frac{I_m^2}{4\pi} \left[\pi - \frac{\sin 2\pi - \sin 0}{2} \right]} \\
 &= \sqrt{\frac{I_m^2}{4\pi} [\pi]} \\
 I_{rms} &= \sqrt{\frac{I_m^2}{4}} \Rightarrow \boxed{I_{rms} = \frac{I_m}{2} = 0.5 I_m}
 \end{aligned}$$

Similarly avg value $\boxed{I_{av} = \frac{I_m}{\pi}}$

1) An alternating voltage $e = 200 \sin 314t$ is applied to a device which offers an ohmic resistance of 20Ω to the flow of current in one dirⁿ, while preventing the flow of current in opposite dirⁿ. Calculate RMS value, avg value, over one cycle.

Given:- $V_m = 200\text{ V}$ $e = 200 \sin 314t$
 $R = 20\Omega$ $V = V_m \sin \omega t$
 $\omega = 314$
 $I_m = \frac{V_m}{R} = \frac{200}{20} = 10\text{ A}$


for one cycle,

$$I_{rms} = \frac{I_m}{2} = \frac{10}{2} = 5\text{ A}$$

$$I_{avg} = \frac{I_m}{\pi} = \frac{10}{\pi} = 3.18\text{ A}$$

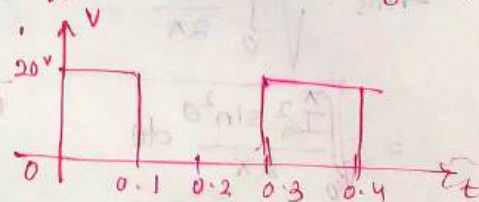2) Compute the avg. & effective values of the square voltage wave

for $0 < t < 0.1$
 $V = 20\text{ V}$
 for $0.1 < t < 0.3$
 $V = 0$



$$T = 0.3 \text{ s}$$

$$V_{\text{avg}} = \frac{1}{T} \int_0^T v \, dt = \frac{1}{0.3} \int_0^{0.1} 20 \, dt$$

$$= \frac{1}{0.3} (20 \times 0.1) = 6.67 \text{ V}$$

$$V^2 = \frac{1}{T} \int_0^T v^2 \, dt = \frac{1}{0.3} \int_0^{0.1} 400 \, dt = \frac{400}{0.3} \times 0.1 = 133.3$$

$$V_{\text{rms}} = 11.5 \text{ V}$$

Complex algebra \Rightarrow

There are diff. forms of representation

- \rightarrow i) Symbolic notation
- ii) Trigonometrical form
- iii) Exponential " iv) Polar form.

$$Z = a + jb \Rightarrow |Z| = \sqrt{a^2 + b^2} \quad \angle Z = \phi = \tan^{-1}\left(\frac{b}{a}\right)$$

angle

$\therefore j = \text{complex operator}$

$a = \text{real}$ $b = \text{img part}$
 $= \text{in-phase}$ $= \text{Quadrature}$

\rightarrow symbol j is used to indicate the counter clockwise rotation of a vector through 90° . It's assigned a value of $\sqrt{-1}$

$$j = \sqrt{-1} \Rightarrow j^2 = -1$$

$$\boxed{\frac{1}{j} = -j}$$

i) Trigonometric form $= E = |E|(\cos \theta + j \sin \theta)$

ii) Exponential " $= e^{\pm j\theta} = \cos \theta \pm j \sin \theta$

$$E = |E| e^{\pm j\theta}$$

iii) Polar form $= E \angle \theta$

Write the equivalent exponential & polar forms of $(3+j4)$.

$$E = a + jb$$

$$\text{Magnitude} = \sqrt{a^2 + b^2} = \sqrt{9 + 16} = 5$$

$$\text{Phase} = \theta = \tan^{-1}\left(\frac{b}{a}\right) = \tan^{-1}\left(\frac{4}{3}\right) = 53.1^\circ$$

$$\text{Exponential form} = 5e^{j53.1^\circ}$$

$$\text{Polar} = 5 \angle 53.1^\circ$$

Addition $\Rightarrow E = E_1 + E_2 = (a_1 + jb_1) + (a_2 + jb_2)$

$$= (a_1 + a_2) + j(b_1 + b_2)$$

$$\text{Magnitude} = \sqrt{(a_1 + a_2)^2 + (b_1 + b_2)^2}$$

$$\text{Phase } \theta = \tan^{-1}\left(\frac{b_1 + b_2}{a_1 + a_2}\right)$$

Subtraction $\Rightarrow E = E_1 - E_2 = (a_1 + jb_1) - (a_2 + jb_2)$

$$= (a_1 - a_2) + j(b_1 - b_2)$$

$$|E| = \sqrt{(a_1 - a_2)^2 + (b_1 - b_2)^2} \quad \theta = \tan^{-1}\left(\frac{b_1 - b_2}{a_1 - a_2}\right)$$

Multiplication \Rightarrow (Rect. form)

$$E = E_1 \times E_2 = (a_1 + jb_1) \times (a_2 + jb_2)$$

$$= (a_1 a_2 - b_1 b_2) + j(a_1 b_2 + b_1 a_2)$$

Division \Rightarrow (Rect. form)

$$E = \frac{E_1}{E_2} = \frac{a_1 + jb_1}{a_2 + jb_2} = \frac{(a_1 + jb_1)(a_2 - jb_2)}{(a_2 + jb_2)(a_2 - jb_2)}$$

$$= \left(\frac{a_1 a_2 + a_1 b_2}{a_2^2 + b_2^2}\right) + j\left(\frac{b_1 a_2 + a_1 b_2}{a_2^2 + b_2^2}\right)$$

29
Add the following vectors given in rectangular form

$$A = 16 + j12 \quad B = -6 + j10.4$$

$$\begin{aligned} Z &= A + B = (16 + j12) + (-6 + j10.4) \\ &= (16 - 6) + j(12 + 10.4) \\ &= 10 + j22.4 \end{aligned}$$

$$\text{mag } |Z| = \sqrt{10^2 + 22.4^2} = 25.5$$


$$\theta = \tan^{-1}\left(\frac{22.4}{10}\right) = 65.95^\circ$$

AC through Pure R, L & C

AC through Pure resistance \Rightarrow

$$\text{Let } V = V_m \sin \omega t \quad (1)$$

I = rms value of the resultant current

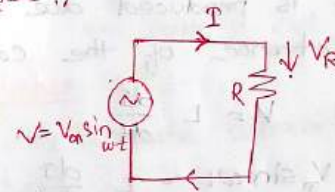

$$\begin{aligned} \text{Voltage drop across } R &= V_R = IR \\ &= I_m \end{aligned}$$

$$V = IR$$

$$\Rightarrow V_m \sin \omega t = IR$$

$$\Rightarrow I = \frac{V_m \sin \omega t}{R} \Rightarrow I = I_m \sin \omega t \quad (2)$$

From eq (1) & (2) ; Both V & I are in same phase.

Instantaneous

$$\text{Power } P = VI$$

$$= (V_m \sin \omega t)(I_m \sin \omega t)$$


$$= V_m I_m \sin^2 \omega t$$

$$= \frac{V_m I_m}{2} (1 - \cos 2\omega t)$$

$$= \frac{V_m I_m}{2} - \frac{V_m I_m \cos 2\omega t}{2} \quad (3)$$

Const.
Part
(Real)

Pulsating Component

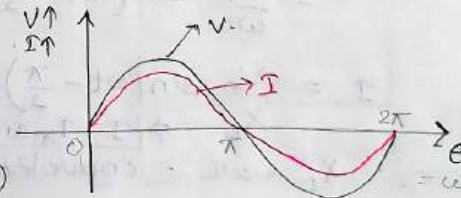

< Same Phase >


for a complete cycle, the avg value of $\frac{V_m I_m \cos \omega t}{2}$ is zero. Hence,

$$P = \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}}$$

$$P = V_{rms} \times I_{rms} \quad \text{--- (4)}$$

AC through Pure Inductance →

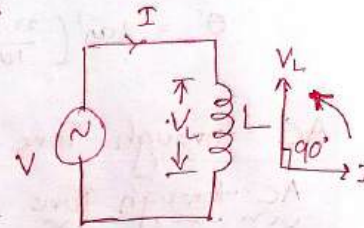Whenever an alternating voltage is applied to a purely inductive coil, a back emf is produced due to self-inductance of the coil.



$$V = L \frac{dI}{dt}$$

$$\Rightarrow V_m \sin \omega t = L \frac{dI}{dt}$$

$$\Rightarrow \frac{dI}{dt} = \frac{V_m}{L} \sin \omega t$$

$$\Rightarrow \int dI = \int \frac{V_m}{L} \sin \omega t dt$$

$$\Rightarrow I = \frac{V_m}{\omega L} (-\cos \omega t)$$


$$= \frac{V_m}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)$$

$$I = \frac{V_m}{X_L} \sin \left(\omega t - \frac{\pi}{2} \right) \quad \text{--- 5(a)}$$

$$X_L \Rightarrow I = I_m \sin \left(\omega t - \frac{\pi}{2} \right) \quad \text{--- 5(b)}$$

$$\therefore X_L = \omega L = \text{inductive reactance}$$
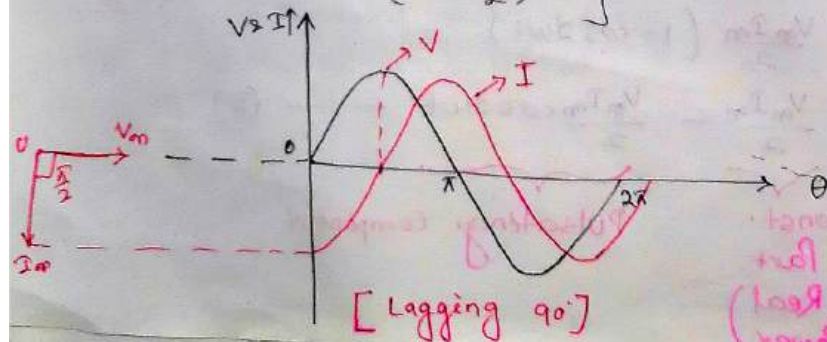
$$\frac{I_m}{X_L} = \frac{V_m}{X_L} \quad \left\{ \begin{array}{l} \text{Value of } I \text{ will be max. when} \\ \sin \left(\omega t - \frac{\pi}{2} \right) = 1 \end{array} \right.$$



Power in Pure inductive ckt:-

24

$$P = VI$$

$$= (V_m \sin \omega t) (I_m \sin(\omega t - \frac{\pi}{2}))$$

$$= V_m I_m \sin \omega t \cdot \sin(\omega t - \frac{\pi}{2})$$

$$= \frac{V_m I_m}{2} [2 \sin \omega t \cdot \sin(\omega t - \frac{\pi}{2})]$$

$$= \frac{V_m I_m}{2} \sin 2\omega t$$

$$= \frac{V_m I_m}{2} [\cos \frac{\pi}{2} - \cos(2\omega t - \frac{\pi}{2})]$$

$$P = 0$$

$$= \frac{V_m I_m}{2} [-\sin 2\omega t] \Rightarrow P = 0 \text{ --- (6)}$$

in pure L ckt.

AC through Pure Capacitance ckt:-

* the ckt containing only a pure capacitor is known as pure capacitor ckt.


* The current leads the voltage by an angle of 90 degree.

* The capacitor works as a storage device.

* If it's connected to the direct supply, it gets charged equal to the value of applied voltage.

* Let alternating Volt. applied
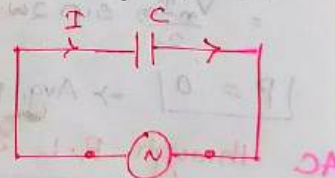
$$V = V_m \sin \omega t \text{ --- (1)}$$



charge of the capacitor at any instant of time

$$\Rightarrow q = CV \text{ --- (2) (a)}$$

$$= C(V_m \sin \omega t) \text{ --- (2) (b)}$$

current flowing through the ckt

$$i = \frac{dq}{dt}$$

$$= \frac{d}{dt} C V_m \sin \omega t \text{ [using eq (2) (b)]}$$

$$= C V_m \omega \cos \omega t = \frac{V_m}{(1/\omega C)} \sin(\omega t + \frac{\pi}{2})$$

$$I = \frac{V_m}{X_c} \sin(\omega t + \frac{\pi}{2}) \quad \text{--- (3)}$$


$$\therefore \left| X_c = \frac{1}{\omega c} \right| = \text{Capacitive reactance}$$

Value of I will be max when $\sin(\omega t + \frac{\pi}{2}) = 1$

$$\text{So } \left[I_m = \frac{V_m}{X_c} \right]$$

$$\text{eq (3) becomes } \left[I = I_m \sin(\omega t + \frac{\pi}{2}) \right] \quad \text{--- (4)}$$

for pure Capacitive ckt

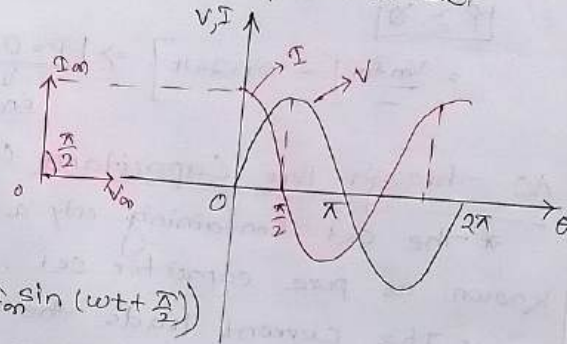

$$P = VI$$

$$= (V_m \sin \omega t) (I_m \sin(\omega t + \frac{\pi}{2}))$$

$$= V_m I_m \sin \omega t \cos \omega t$$

$$= \frac{V_m I_m}{2} [2 \sin \omega t \cos \omega t]$$

$$= \frac{V_m I_m}{2} \sin 2\omega t$$

$$|P = 0| \rightarrow \text{Avg. power in capacitive ckt} = \text{Zero}$$


AC through R-L Series ckt

* A Circuit that contains a pure resistance (R) connected in series with a coil having pure inductance (L) is known as RL Series ckt.

* Let an AC supply vol 'V' is applied, the current I flows in the circuit.

Q

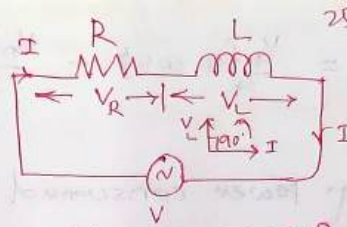$V_R = IR$
 = Voltage drop across
 R
 (in phase with I)



$V_L = I \cdot X_L$
 = Voltage drop across coil
 (ahead of I by 90°)

ΔOAB

$$V = \sqrt{V_R^2 + V_L^2}$$

$$= \sqrt{(IR)^2 + (IX_L)^2}$$

$$= I \sqrt{R^2 + X_L^2}$$

$$\Rightarrow \frac{V}{I} = \sqrt{R^2 + X_L^2} \Rightarrow Z = \sqrt{R^2 + X_L^2}$$

Impedance, unit = Ω

$$[(\text{Impedance})^2 = (\text{resistance})^2 + (\text{reactance})^2]$$

Phase angle: — In RL series circuit, the I lags voltage by 90° angle known as phase angle.

$$\tan \theta = \frac{V_L}{V_R} = \frac{IX_L}{IR} = \frac{X_L}{R} \text{ or}$$

$$\phi = \tan^{-1} \left(\frac{X_L}{R} \right)$$

Power :-

$$V = V_m \sin \omega t \quad \text{--- (1)}$$

$$i = I_m \sin(\omega t - \phi) \quad \therefore I_m = \frac{V_m}{Z}$$

$$P = Vi$$

$$= (V_m \sin \omega t)(I_m \sin(\omega t - \phi))$$

$$= \frac{V_m I_m}{2} [2 \sin \omega t \sin(\omega t - \phi)]$$

$$= \frac{V_m I_m}{2} [\cos(\omega t - \omega t + \phi) - \cos(\omega t + \omega t - \phi)]$$

$$\Rightarrow P = \frac{V_m I_m \cos \phi}{2} - \frac{V_m I_m \cos (2\omega t - \phi)}{2}$$

Avg power consumed $P = \frac{V_m I_m \cos \phi}{2}$

$$= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \phi$$

$$= V_{rms} I_{rms} \cos \phi$$

$$\Rightarrow P = VI \cos \phi$$

$\therefore \cos \phi$ = power factor of the circuit.

- ⑥ Power factor \rightarrow It may be defined as
- i) cosine of the angle of lead or lag
 - ii) the ratio $\frac{R}{Z} = \frac{\text{resistance}}{\text{impedance}}$

iii) $\cos \phi = \frac{\text{true power (W)}}{\text{Apparent Power (VA)}} = \frac{\text{watt}}{\text{Volt. amp}} = \frac{W}{VA}$

⑥ Active power (Φ or W)

Power which is actually dissipated in the circuit resistance

$$P = I^2 R = VI \cos \phi \text{ watts.}$$

⑥ Reactive Power (Q)

Power developed in the inductive reactance of the circuit.


$$Q = I^2 X_L = I^2 Z \sin \phi = I \cdot (IZ) \sin \phi = VI \sin \phi$$

⑥ Apparent Power (S)

Product of rms values of applied voltage & circuit current.

$$S = VI = (IZ) \cdot I = I^2 Z$$

$$S = \sqrt{P^2 + Q^2}$$

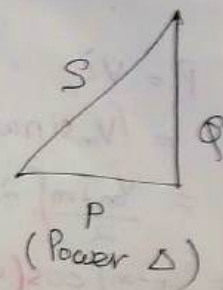

① In a series circuit containing pure resistance & a pure inductance, the current & voltage are expressed as:

$$i(t) = 5 \sin(314t + \frac{2\pi}{3}) \text{ \& } V(t) = 15 \sin(314t + \frac{5\pi}{6})$$

- What's the impedance of the ckt?
- What's the value of the resistance?
- What's the inductance in henry?
- What's the avg power drawn by ckt?
- What's the power factor?

$$i(t) = 5 \sin(314t + \frac{2\pi}{3}) \Rightarrow I_m = 5, \phi = \frac{2\pi}{3} = 120^\circ$$

$$V(t) = 15 \sin(314t + \frac{5\pi}{6}) \Rightarrow V_m = 15, \phi = \frac{5\pi}{6} = 150^\circ$$

$$a) \text{ Impedance } Z = \frac{V_m}{I_m} = 3 \Omega$$

Phase diff. bet $V(t)$ & $i(t)$ = 30° . It means Current lags behind Voltage by 30° i.e. RL ckt.

$$b) \frac{R}{Z} = \cos \phi \Rightarrow R = Z \cos \phi$$

$$= 3 \cos 30^\circ$$

$$= 2.598 \approx \underline{\underline{2.6 \Omega}}$$

$$c) X_L = \omega L \text{ or } Z \sin \phi$$

$$= 3 \sin 30^\circ = 1.5$$

$$\Rightarrow \cancel{2\pi f L} = 1.5 \quad \omega L = 1.5$$

$$\Rightarrow \cancel{2\pi \times} \Rightarrow 314 L = 1.5 \Rightarrow L = \frac{1.5}{314} = 0.00477 \text{ H}$$

$$\text{or } \underline{\underline{4.77 \text{ mH}}}$$



$$d) P = I^2 R = I_{rms}^2 R = \left(\frac{5}{\sqrt{2}}\right)^2 \times 2.6$$

$$= \frac{25}{2} \times 2.6 = 32.5 \text{ W}$$

$$e) \text{ Power factor} = \cos \phi = \cos 30^\circ = \frac{\sqrt{3}}{2} = 0.866$$

(lag)

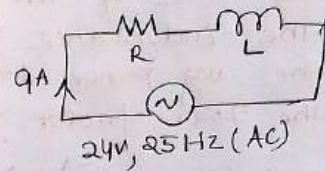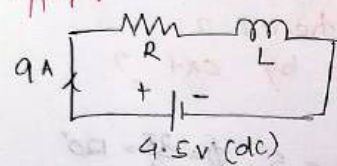2) The potential diff. measured across a coil is 4.5 V, when it carries a direct current of 9 A. The same coil when carries an alternating current of 9 A at 25 Hz, the potential diff. is 24 V. Find the current, the power & the p.f. when it's supplied by 50 V, 50 Hz supply.



i) for dc,

$$f_{\text{req}} = 0$$

$$R = \frac{V}{I} = \frac{4.5}{9} = 0.5 \Omega$$

ii) when ac, $I_{\text{rms}} = 9 \text{ A}$,

$$Z = \frac{V}{I} = \frac{24}{9} = 2.66 \Omega$$

$$Z = \sqrt{R^2 + X_L^2} \Rightarrow 2.66 = \sqrt{0.5^2 + X_L^2} \quad \left[X_L = \sqrt{Z^2 - R^2} \right]$$

$$\Rightarrow X_L = \sqrt{2.66^2 - 0.5^2} = 2.62 \Omega$$

$$\Rightarrow 2\pi fL = 2.62$$

$$\Rightarrow L = \frac{2.62}{2\pi \times 25} = 0.0167 \text{ H}$$

At 50 V, 50 Hz,

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.0167 = 5.24 \Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{(0.5)^2 + (5.24)^2} = 5.26 \Omega$$

$$I = \frac{V}{Z} = \frac{50}{5.26} = 9.5 \text{ A}$$

$$P = I^2 R = (9.5)^2 \times 0.5 = 45 \text{ W}$$

$$\text{P.f.} = \cos \phi = \frac{R}{Z} = \frac{0.5}{5.26} = 0.095$$

3) In a particular R-L series circuit a voltage of 10V at 50 Hz produces a current of 700 mA while the same voltage at 75 Hz produces 500 mA. What are the values of R & L?

Solⁿ $V = 10V, I = 700 \text{ mA}$
 $f = 50 \text{ Hz},$

i) $Z = \sqrt{R^2 + X_L^2} \therefore X_L = 2\pi fL = 2\pi \times 50 L$
 $= 100\pi L$

$$I = \frac{V}{Z} = \frac{10}{\sqrt{R^2 + (100\pi L)^2}}$$

$$\Rightarrow 700 \times 10^{-3} = \frac{10}{\sqrt{R^2 + (100\pi L)^2}} \Rightarrow \left(\sqrt{R^2 + (100\pi L)^2} \right) = \frac{10}{700 \times 10^{-3}}$$

$$\Rightarrow R^2 + (100\pi L)^2 = \left(\frac{10}{700 \times 10^{-3}} \right)^2$$

$$\Rightarrow R^2 + 98696 L^2 = 204.08 \quad (1)$$

ii) $f = 75 \text{ Hz} \quad I = 500 \text{ mA}$

$$I = \frac{V}{Z} = \frac{10}{\sqrt{R^2 + (2\pi \times 75 L)^2}}$$

$$\Rightarrow 500 \text{ mA} = \frac{10}{\sqrt{R^2 + (150\pi L)^2}}$$

$$\Rightarrow \left(\frac{10}{500 \times 10^{-3}} \right)^2 = R^2 + (150\pi L)^2 \Rightarrow 400 = R^2 + 222066 L^2 \quad (2)$$

\therefore Subtracting eq (1) from (2),

$$R^2 + 222066 L^2 = 400$$

$$- R^2 + 98696 L^2 = 204.08$$

$$\hline 123370 L^2 = 195.92$$

$$\Rightarrow L^2 = 0.001588$$

$$L = 0.0398 \text{ H}$$

$$\text{or } 39.8 \text{ mH} \approx 40 \text{ mH}$$

Putting this value in eqⁿ (2)

$$R^2 + 222066(0.0398)^2 = 400$$

$$\Rightarrow R^2 = 400 - 351.76$$
$$= 48.24$$

$$R = 6.95 \Omega$$

4) A series ckt consists of a resistance of 6Ω & an inductive reactance of 8Ω . A potential diff. of $141.4V$ (rms) is applied to it. At a certain instant the applied voltage is $100V$ & is increasing. Find at this current,
i) the current ii) the voltage drop across the resistance iii) voltage drop across inductive reactance.

$$R = 6\Omega, X_L = 8\Omega, V_{rms} = 141.4V$$
$$V = 100V$$

$$Z = R + jX_L = 6 + j8 = 10 \angle 53.13^\circ$$
$$\phi = \tan^{-1}\left(\frac{8}{6}\right) = 53.13^\circ$$

$$V_m = \sqrt{2} V_{rms} = 141.4 \sqrt{2} = 199.96 \approx 200V$$

$$V = V_m \sin \omega t = 200 \sin \omega t \quad \text{--- (1)}$$

$$I_m = \frac{V_m}{Z} = \frac{200}{10} = 20$$

Currents lags behind voltage by 53.13°

$$\text{So } i = 20 \sin(\omega t - 53.13^\circ) \quad \text{--- (2)}$$

i) when the voltage is $100V$

$$V = 200 \sin \omega t$$

$$\Rightarrow 100 = 200 \sin \omega t$$

$$\Rightarrow \omega t = \sin^{-1}\left(\frac{100}{200}\right) = 30^\circ$$

So current at this point from eqⁿ (2)

$$i = 20 \sin(30^\circ - 53.13^\circ)$$

$$= -7.856 A$$

i) Voltage drop across R

10
28 1

$$= iR = -7.856 \times 6$$

$$= -47.13 \text{ V}$$

ii) Voltage drop across inductive reactance

$$V_L = I_m X_L$$

$$= 20 \times 8 = 160 \text{ V}$$

$$V_L = iX_L = 20 \sin(\omega t - 53.13) \times 8 \angle 90^\circ$$

$$= 20 \angle -53.13 \times 8 \angle 90^\circ$$

$$= 160 \angle 90^\circ - 53.13^\circ$$

$$= 160 \angle 36.87^\circ = 160 \angle 36.9^\circ$$

Hence at $\omega t = 30^\circ$, the voltage drop is

$$V_L = 160 \sin(30^\circ + 36.9^\circ)$$

$$= 147.17 \text{ V}$$

5) A 200V, 50 Hz, inductive circuit takes a current of 10 A, lagging 30 degree. Find (i) resistance
ii) reactance iii) inductance of coil.

$$V = 200 \text{ V}, f = 50 \text{ Hz}, I = 10 \text{ A}, \phi = 30^\circ (\text{lag})$$

$$Z = \frac{V}{I} = \frac{200}{10} = 20 \Omega$$

$$i) R = Z \cos \phi = 20 \cos 30^\circ = 17.32 \Omega$$

$$ii) X_L = Z \sin \phi = 20 \sin 30^\circ = 10 \Omega$$

$$iii) X_L = 2\pi fL \Rightarrow L = \frac{X_L}{2\pi f} = \frac{10}{2 \times 3.14 \times 50} = 0.0318 \text{ H}$$

6) A Capacitor of capacitance $79.5 \mu\text{F}$ is connected in series with a non-inductive resistance of 30Ω across a 100V, 50 Hz. Find (i) impedance ii) current
iii) Phase angle iv) Equation for instant. value of i

$$C = 79.5 \times 10^{-6} \text{ F}, R = 30, V = 100, f = 50$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2 \times 3.14 \times 50 \times 79.5 \times 10^{-6}} = 40 \Omega$$

$$i) Z = \sqrt{R^2 + X_C^2} = \sqrt{30^2 + 40^2} = 50 \Omega$$

$$ii) I = \frac{V}{Z} = \frac{100}{50} = 2 A$$

$$iii) \phi = \tan^{-1} \left(\frac{X_C}{R} \right) = \tan^{-1} \left(\frac{40}{30} \right) = 53^\circ \text{ lead}$$

$$iv) I = \frac{I_m}{\sqrt{2}} \Rightarrow I_m = \sqrt{2} I = \sqrt{2} \times 2 = 2.83 A$$

$$\omega = 2\pi f = 2 \times 3.14 \times 50 = 314 \text{ rad/sec}$$

$$i = I_m \sin(\omega t + \phi)$$

$$= 2.83 \sin(314t + 53^\circ)$$

⑦ In a given RL circuit, $R = 3.5 \Omega$ & $L = 0.1 \text{ H}$ ¹⁰
 Find (i) the Current through the circuit and
 (ii) Power factor if a 50 Hz voltage $V = 220 \angle 30^\circ$ is
 applied across the circuit.

$$R = 3.5 \Omega, L = 0.1 \text{ H}, f = 50 \text{ Hz},$$

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.1 = 31.42 \Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{(3.5)^2 + (31.42)^2} = 31.6$$

$$Z = 31.6 \angle \tan^{-1}\left(\frac{31.42}{3.5}\right) = 31.6 \angle 83.65^\circ$$

$$I = \frac{V}{Z} = \frac{220 \angle 30^\circ}{31.6 \angle 83.65^\circ} = 6.96 \angle -53.65^\circ$$

$$\text{Phase angle bet } V \text{ \& } i = 53.65 + 90^\circ = 83.65^\circ (\text{lag})$$

$$P.f = \cos 83.65 = 0.11 (\text{lag})$$

⑧ A 2-element Series circuit is connected across
 an ac source $e = 200\sqrt{2} \sin(\omega t + 20^\circ) \text{ V}$. The current
 in the circuit is found as $i = 10\sqrt{2} \cos(314t - 25^\circ)$. Find
 the parameters of the circuit.

$$e = 200\sqrt{2} \sin(\omega t + 20^\circ) = 200\sqrt{2} \angle 20^\circ$$

$$i = 10\sqrt{2} \cos(314t - 25^\circ)$$

$$= 10\sqrt{2} \sin(314t - 25^\circ + 90^\circ)$$

$$= 10\sqrt{2} \sin(314t + 65^\circ)$$

$$= 10\sqrt{2} \angle 65^\circ$$

$$Z = \frac{e}{i} \text{ or } \frac{V}{i} = \frac{200\sqrt{2} \angle 20^\circ}{10\sqrt{2} \angle 65^\circ} = 20 \angle -45^\circ = 14.1 - j14.1$$


$$R = 14.1 \Omega \quad X_C = 14.1 \Omega$$

$$\Rightarrow \frac{1}{2\pi fC} = 14.1$$


$$C = \frac{1}{2\pi \times 50 \times 14.1} = 226 \mu\text{F}$$

AC through RC \rightarrow < Series RC circuits >

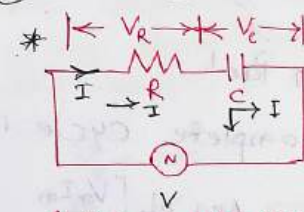* A circuit that contains pure R connected in series with a pure C is known as RC Series Ckt.



< RC Series Ckt >

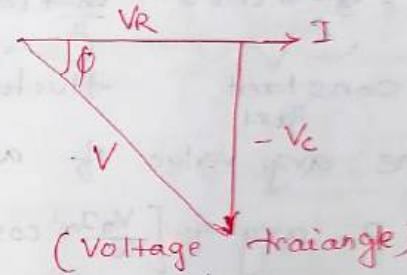

Drop across R = $V_R = IR$ (Phasor diagram)
(in phase with I)

Drop across Capacitor $V_C = IX_C$ [lagging I by $\frac{\pi}{2}$]
 $\therefore X_C = \frac{1}{2\pi fC}$

As X_C is taken -ve, V_C is shown along -ve direction of Y-axis.

$$\text{Now } V = \sqrt{V_R^2 + (-V_C)^2} = \sqrt{(IR)^2 + (-IX_C)^2}$$

$$= I \sqrt{R^2 + X_C^2}$$

$$\Rightarrow \frac{V}{I} = \sqrt{R^2 + X_C^2} \Rightarrow \boxed{Z = \sqrt{R^2 + X_C^2}}$$

Impedance of Series RC circuit

From voltage Δ , it is found that I leads V by an angle ϕ , this angle is called phase angle.

$$\tan \phi = \frac{-V_C}{V_R} = \frac{-IX_C}{IR} = \frac{-X_C}{R}$$

$$\text{or } \phi = \tan^{-1} \left(\frac{-X_C}{R} \right)$$

\rightarrow If $V = V_m \sin \omega t$

$$i = I_m \sin(\omega t + \phi)$$

Then $P = Vi$

$$= (V_m \sin \omega t) (I_m \sin(\omega t + \phi))$$

$$= \frac{V_m I_m}{2} \left[2 \sin \omega t \cdot \sin(\omega t + \phi) \right]$$

$$= \frac{V_m I_m}{2} \left[\cos(\omega t + \omega t - \phi) - \cos(\omega t + \omega t + \phi) \right]$$

$$\sin A \cdot \sin B = \frac{\cos(A+B) - \cos(A-B)}{2}$$

$$= \underbrace{\frac{V_m I_m}{2} \cos \phi}_{\text{Constant Part}} - \underbrace{\frac{V_m I_m}{2} \cos(2\omega t + \phi)}_{\text{Fluctuation Part}}$$

The avg. value of a complete cycle is

$$P = \text{avg of } \left[\frac{V_m I_m}{2} \cos \phi \right] - \text{Avg of } \left[\frac{V_m I_m}{2} \cos(2\omega t + \phi) \right]$$

$$= \frac{V_m I_m}{\sqrt{2}} \cos \phi - 0$$

$$P = V_{rms} I_{rms} \cos \phi$$

$$P = VI \cos \phi \quad \text{where } \cos \phi = \text{Power factor of the ckt.}$$

1) In a circuit, the applied voltage is 100V and is found to lag the current of 10A by 30°. i) Is the p.f. lagging or leading? ii) What's the value of P.F. iii) Is the circuit inductive or capacitive? iv) What is the value of active & reactive power in the circuit?

Given $V = 100V$, $I = 10A$, $\phi = 30^\circ$

i) ~~As~~ given voltage is lagging behind I, so current leads voltage. P.f. is leading.

ii) $P.F = \cos \phi = \cos 30^\circ = 0.866$ (lead)

iii) As I leads V, ckt is capacitive.

iv) Active power = $VI \cos \phi$
 $= 100 \times 10 \times 0.866 = 866 \text{ W}$


Reactive power = $VI \sin \phi$
 $= 100 \times 10 \times \sin 30^\circ = 500 \text{ VAR}$

Q A tungsten filament bulb rated at 500 W, 100 V is to be connected to series with a capacitance across 220 V, 50 Hz supply. Calculate a) the value of capacitor such that the voltage & power consumed by the bulb are according to the rating of the bulb, b) the power factor of current drawn from the supply. c) draw the phasor diagram.

$$V_R = 100 \text{ V}$$

$$P = VI \Rightarrow 500 = 100I$$

$$I = \frac{500}{100} = 5 \text{ A}$$

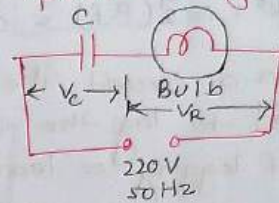

$$a) V_C = \sqrt{220^2 - 100^2} \Rightarrow IX_C = 195.9 \approx 196$$

$$\Rightarrow 5X_C = 196$$

$$\Rightarrow X_C = 39.2 \Omega$$

$$\Rightarrow \frac{1}{2\pi fC} = 39.2 \Rightarrow C = \frac{1}{2\pi \times 50 \times 39.2}$$

$$= 8.12 \times 10^{-5} \text{ F}$$


$$\approx 81.2 \mu\text{F}$$

$$b) \text{ p.f} = \cos \phi = \frac{V_R}{V}$$

$$= \frac{100}{220} = 0.454$$

$$\text{p.f} = 0.454$$

c) Phasor diagram \rightarrow

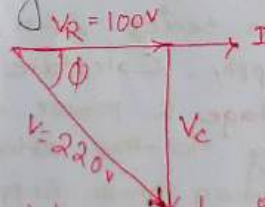

Q A pure resistance of 50 Ω is in series with a pure capacitance of 100 μF . The series comb is connected across 100 V, 50 Hz supply. find a) the impedance b) I c) p.f d) phase angle e) voltage across R, f) Vol. across C.

$$R = 50 \Omega, C = 100 \mu\text{F}, V = 100 \text{ V}, f = 50 \text{ Hz}$$

$$a) Z = \sqrt{R^2 + X_C^2} \quad \therefore X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}}$$

$$= \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} = \frac{10^6}{100\pi \times 100} = 32.52$$

$$Z = \sqrt{50^2 + 32^2} = 59.4 \Omega$$

$$b) I = \frac{V}{Z} = \frac{100}{59.4} = 1.683 \text{ A}$$

$$c) P.f = \frac{R}{Z} = \frac{50}{59.4} = 0.842$$

$$d) \phi = \cos^{-1}(P.f) = \cos^{-1}(0.842)$$

4) On a circuit, the applied voltage is 100V and found to lag the current of 10 A by 30°. i) Is the P.f lagging or leading? ii) What is the value of P.f. iii) Is the circuit inductive or capacitive. iv) What's the value of active & reactive power in the circuit.

$$\phi = 30^\circ (\text{lag}) \quad I = 10 \text{ A}$$

i) Current is leading the voltage by 30°. Hence P.f is leading.

$$ii) P.f = \cos \phi = \cos 30^\circ = 0.866$$



iii) As I leads V , circuit is capacitive.

$$iv) \text{Active Power } P = VI \cos \phi$$

$$= 100 \times 10 \times 0.866 = 866 \text{ W}$$

$$v) \text{Reactive Power } Q = VI \sin \phi = 100 \times 10 \times \sin 30^\circ = 500 \text{ VAR}$$

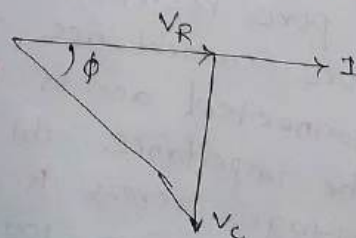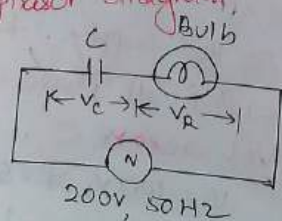5) A tungsten filament bulb rated at 500 W, 100 V is to be connected to series with a capacitor across 200 V, 50 Hz supply. Calculate a) value of C such that the voltage & power consumed by the bulb are according to the rating of bulb, b) the P.f of the I drawn from supply, c) Draw the phasor diagram.



$$V = 200 \text{ V}, f = 50 \text{ Hz}, P = 500 \text{ W}, V_R = 100$$

$$V_C = \sqrt{V^2 - V_R^2} = \sqrt{200^2 - 100^2} = 196$$


$$\Rightarrow IX_C = 196 \rightarrow X_C = \frac{196}{5} = 39.2$$


$$\rightarrow \frac{1}{2\pi fC} = 39.2 \rightarrow \frac{1}{2\pi \times 50 \times 39.2} = C$$

$$\Rightarrow \boxed{C = 81 \mu\text{F}}$$

$$b) \text{ P.f} = \cos \phi = \frac{V_R}{V} = \frac{100}{200} = 0.455$$

c) Phasor diagram =

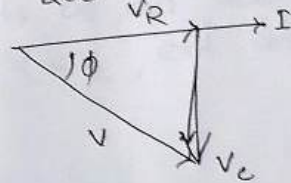

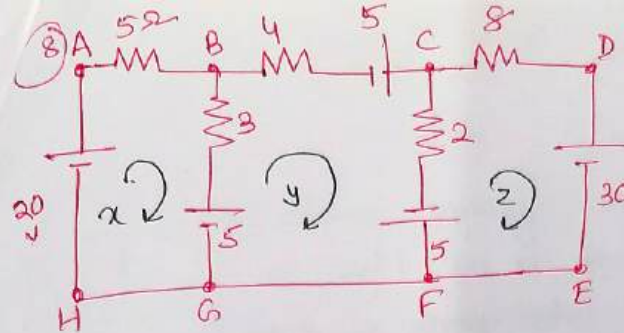

Find the current supplied by each battery in the shown ckt.

Using KVL in ABGHA

$$20 - 5x - 3(x-y) - 5 = 0$$

$$\Rightarrow 15 - 5x - 3x + 3y = 0 \Rightarrow 8x - 3y = 15 \quad \text{--- (1)}$$

in BCFGB,

$$5 - 3(y-x) - 4y + 5 - 2(y-z) + 5 = 0$$

$$\Rightarrow 15 - 3y + 3x - 4y - 2y + 2z = 0$$

$$\Rightarrow 15 + 3x - 9y + 2z = 0 \Rightarrow 3x - 9y + 2z = -15 \quad \text{--- (2)}$$

in CDEFC,

$$-5 - 2(z-y) - 8z + 30 = 0$$

$$\Rightarrow -35 - 2z + 2y - 8z = 0$$

$$\Rightarrow -10z + 2y = 35 \Rightarrow 2y - 10z = 35 \quad \text{--- (3)}$$

Solving eqⁿ (1), (2), (3)

$$8x - 3y = 15$$

$$3x - 9y + 2z = -15$$