

## Experiment – 8

### Aim of the experiment –

To study the operation of SR and D flip flops.

### Apparatus required -

- Flip flop kit
- Connecting wires



### Theory -

#### SR flip flop –

A SR flip flop is an arrangement of logic gates that maintain a stable output even after the inputs are turned off. This simple flip flop circuit has a set input(S) and a reset input (K). The set input causes the output 0(top output) and 1(bottom output). The reset causes the vice - versa (top – 1bottom – 0).

#### S R Truth table -

clk	S	R	$Q_{n+1}$	$\bar{Q}_{n+1}$	Operatios
0	x	x	$Q_n$	$\bar{Q}_n$	No change
1	0	0	$Q_n$	$\bar{Q}_n$	No change
1	0	1	0	1	Reset
1	1	0	1	0	Set
1	1	1	1	1	Invalid

  

### D flip flop –


It is also known as a "data" or "delay" flip - flop. The D flip-flop captures the value of the D-input at a definite portion of the clock cycle (low to high or high to low). The output shows the current stored values.

### D Truth table –

clk	D	$Q_{n+1}$	$\bar{Q}_{n+1}'$	condition
0	X	$Q_n$	$Q_n'$	No change
1	0	0	1	Reset
1	1	1	0	Set
 
### J K flip flop –

The JK flip-flop augments the behavior of the SR flip-flop (J=Set, K=Reset) by interpreting the  $J = K = 1$  condition as a "flip" or toggle command. The combination  $J = 1, K = 0$  is a command to set the flip-flop; the combination  $J = 0, K = 1$  is a command to reset the flip-flop; and the combination  $J = K = 1$  is a command to toggle the flip-flop.



## J K Truth table –

J	K	$Q_{n+1}$	$\overline{Q}_{n+1}'$	CONDITION
x	x	$Q_n$	$Q_n'$	No change
0	0	$Q_n$	$Q_n'$	No change
0	1	0	1	Reset
1	0	1	0	Set
1	1	$Q_n'$	$Q_n$	Toggle

### **OBSERVATION:**

Draw the observation table as per truth table in high and low format.

### **CONCLUSION:**