

## Experiment – 5

### Aim of the experiment

To design and implement combinational logic circuit to test half adder, full adder, half subtractor and full subtractor.

### Objective –

To verify and implement the combinational logic circuit of half adder, full adder, half subtractor and full subtractor.

### Apparatus required –


Serial No	Items	Specifications
1..	Project Board	
2.	IC's 7404 7408 7432 7486	Hex Inverter Quad 2 I/p AND gate Quad 2 I/P OR gate Quad 2 I/P Ex-or gate

### Theory –

1. Half adder - It can add 2 bits.

Expression for sum :-  $S = A'B + AB' = A \oplus B$

Expression for carry :-  $C = AB$

 


Truth Table for Half Adder:

A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 2.Full adder- It can add 3 bits.

Expression for sum =

$$\begin{aligned} S &= A'B'C + A'BC' + AB'C' + ABC \\ &= C(A'B' + AB) + C'(A'B + AB') \\ &= C(A \oplus B)' + C'(A \oplus B) \\ &= A \oplus B \oplus C \end{aligned}$$



Expression for carry -

$$\begin{aligned} C &= A'BC + AB'C + ABC' + ABC \\ &= A(CB' + BC) + BC = A(B \oplus C) + BC \end{aligned}$$

Truth Table for Full Adder:


3.Half subtractor – It can subtract 2 bits.

Truth Table For Half Subtractor:

A	B	Difference	Borrow
0	0	0	0
0	1	1	1
0	0	1	0
0	1	0	0

Expression for difference,  $\text{Diff} = A' B + A B' = A \oplus B$

 
Expression for borrow,  $\text{Borrow} = A' B$



4.Full subtractor —: It can subtract 3 bits.

Truth Table for Full Subtractor:

A	B	C	Difference	Carry
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

 

$$\begin{aligned}
 \text{Expression for difference, Diff} &= A' B' C + A B C' + A B' C + A B C \\
 &= C (A' B' + A B) + C' (A' B + A B') = C(A \oplus B)' + C'(A \oplus B) \\
 &= A \oplus B \oplus C
 \end{aligned}$$

$$\begin{aligned}
 \text{Expression for borrow, Borrow} &= A' B' C + A' B C' + A' B C + A B C \\
 &= C(A \oplus B)' + A' B
 \end{aligned}$$

**Observation-**

(Draw the observation tables in High and Low format)

1.Adder:

i)Half adder:

ii)Full adder:

2.Subtractor:

i)Half Subtractor:

ii)Full Subtractor:

**Conclusion-**